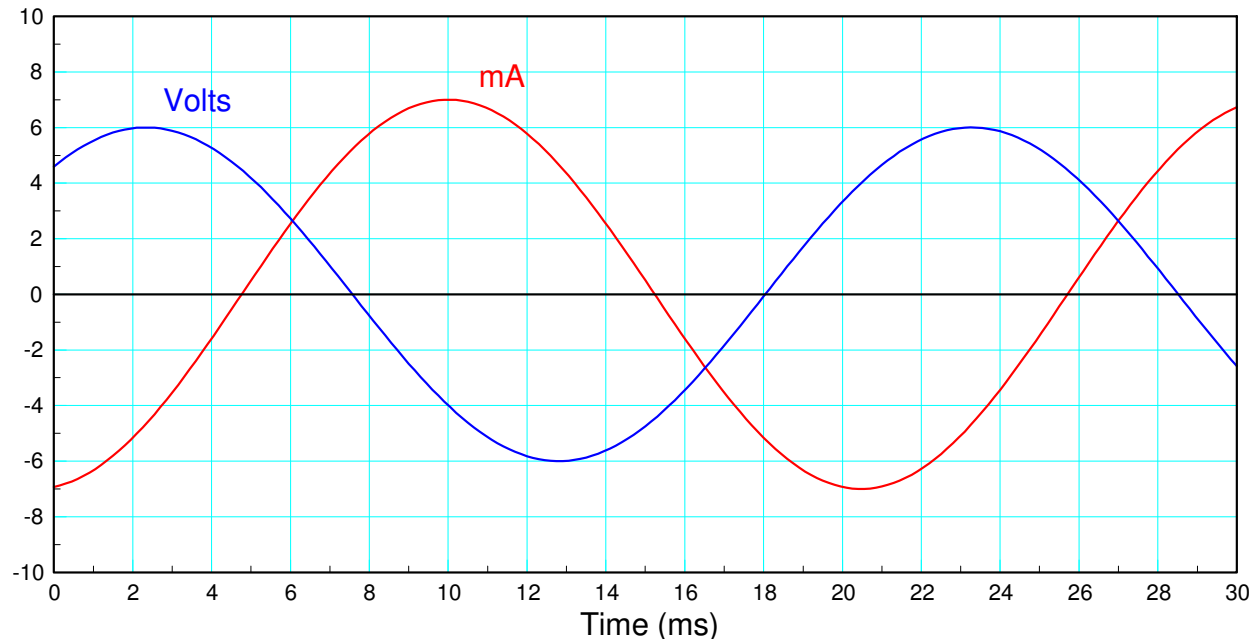


ECE 111 - Homework #13

ECE 311 Circuits II - Phasors


Phasor Voltages

- Express V and I as phasors (i.e. as complex numbers)
 - From this, determine the impedance, $Z = V/I$




Phasor Impedances


- Determine the impedance, Z_{ab}

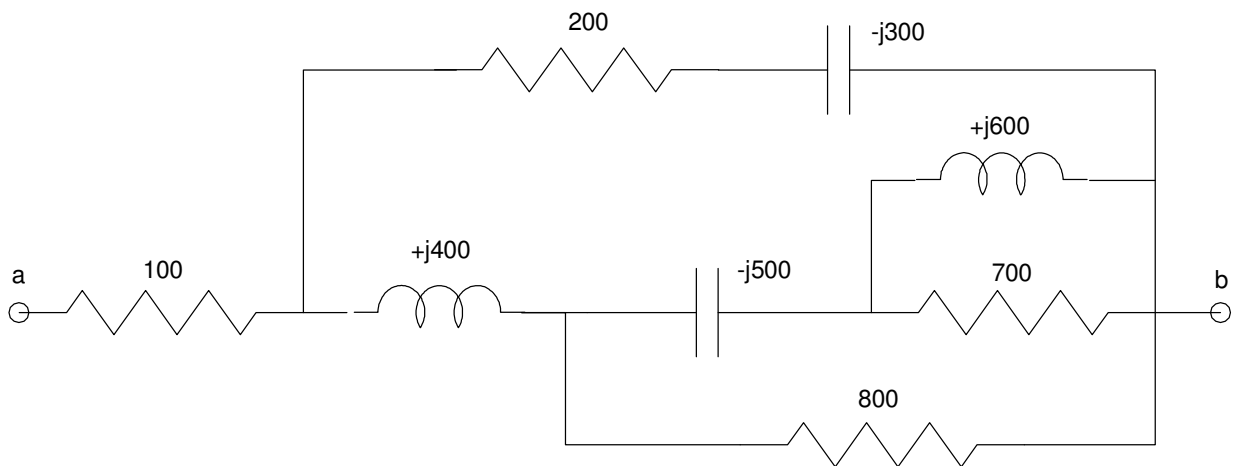

3) Determine the impedance, Z_{ab}

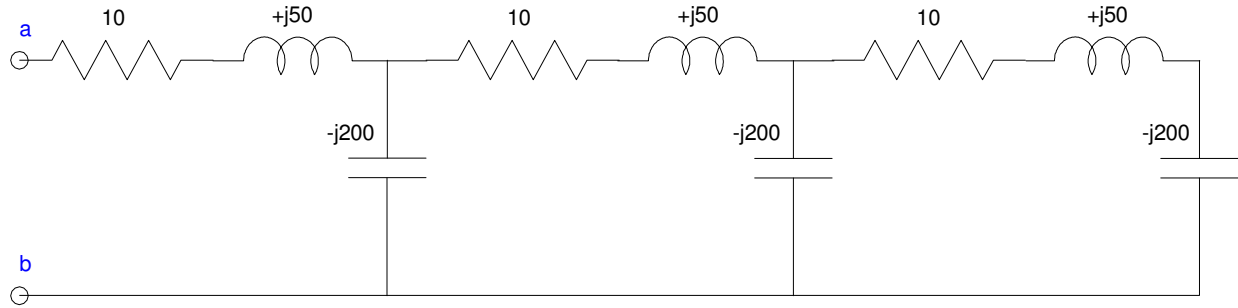

Voltage Nodes with Phasors

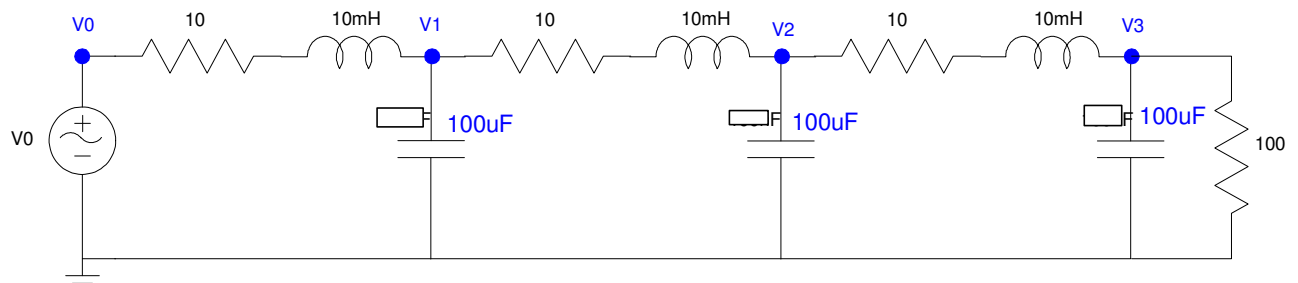

4) Assume $V_0 = 10$.

- a) Determine the impedances of each element at 0 rad/sec
- b) Write the voltage node equations
- c) Solve for V_1 , V_2 , and V_3 .

5) Check your results in CircuitLab

6) Assume $V_0 = 10 \sin(40t)$ $10V, 40 \text{ rad/sec sine wave } (6.36Hz)$

- a) Determine the impedances of each element at 40 rad/sec
- b) Write the voltage node equations
- c) Solve for V_1 , V_2 , and V_3 as complex numbers
- d) Express V_1 , V_2 , and V_3 in terms of sine and cosine function:
- hint: $V_1 = a + jb$ (phasor representation) means $V_1(t) = a \cos(40t) - b \sin(40t)$

7) Check your results in CircuitLab using a transient simulation for 500ms (time step = 5us).