


ECE 111 - Homework #10

ECE 311 Circuits II - Capacitors & the Heat Equation

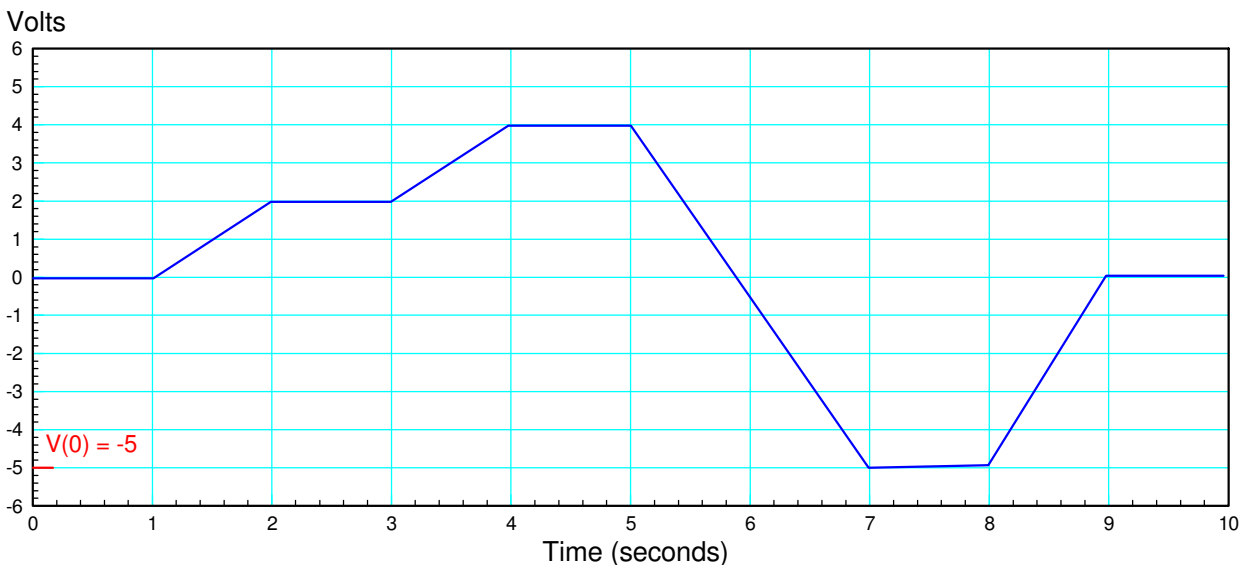
1) Assume the current flowing through a one Farad capacitor is shown below. Sketch the voltage. Assume $V(0) = 0$. The voltage is the integral of the current (capacitors are integrators)

$$V = \frac{1}{C} \int I \cdot dt$$

Assume the initial voltage on the capacitor is -5V.



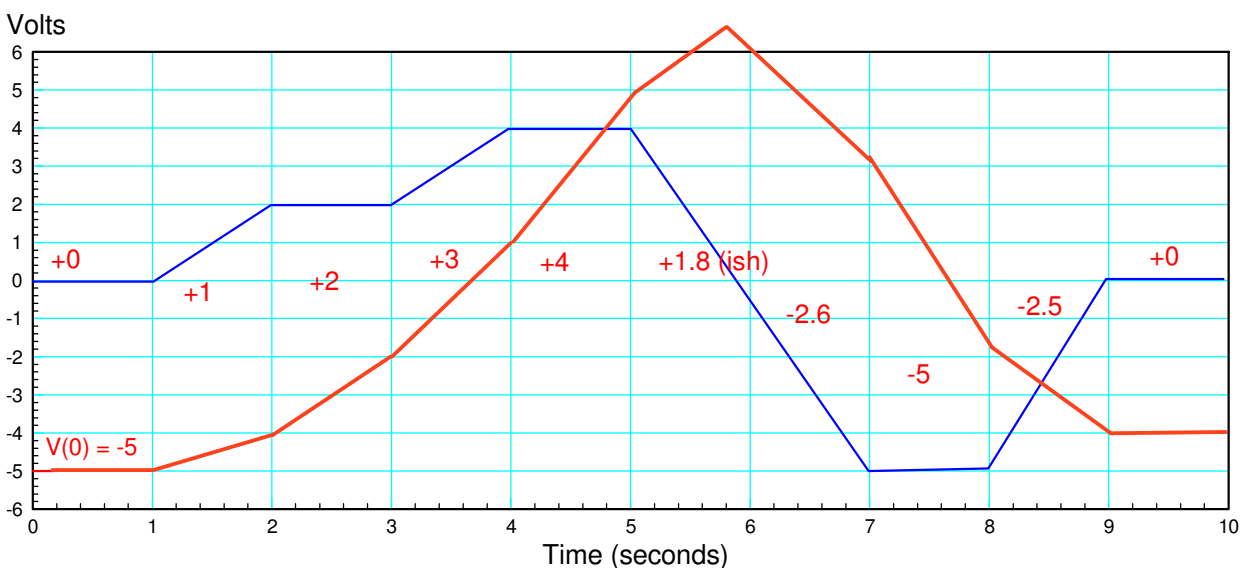
The integral is the area under the curve (positive goes up, negative goes down)



1-Stage RC filter:

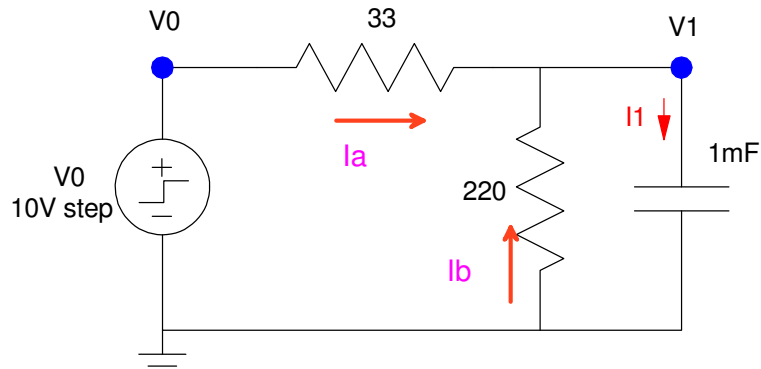2) Write the differential equation that describe this circuit. Note:

$$I_1 = C \frac{dV_1}{dt} = \sum (\text{current to node } V_1)$$



$$I_1 = C \frac{dV_1}{dt} = I_a + I_b$$

$$I_1 = 0.001 V_1' = \left(\frac{V_0 - V_1}{33} \right) + \left(\frac{0 - V_1}{220} \right)$$


Doing some algebra

$$V_1' = 30.303 V_0 - 34.848 V_1$$


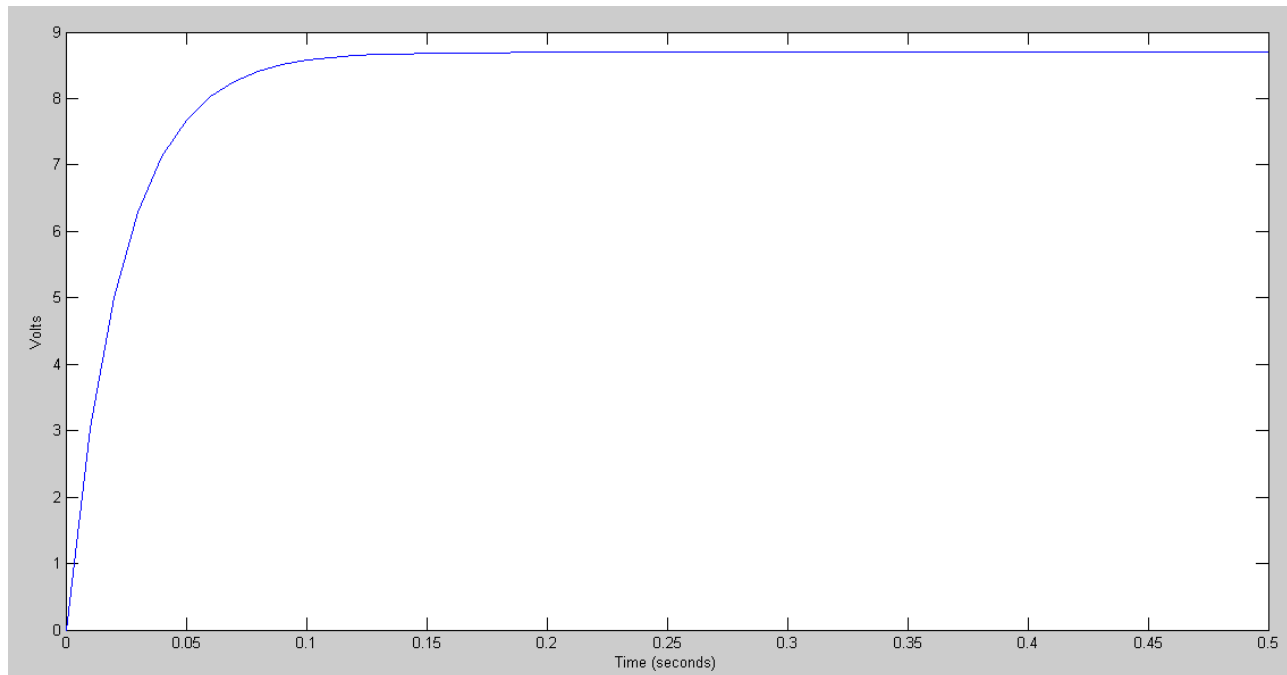
3) Find and plot $V_1(t)$ for 1/2 second using Matlab.

Matlab Code:

```
V0 = 10;  
V1 = 0;  
dt = 0.01;  
t = 0;  
  
y = [V1];  
  
while(t < 0.5)  
  
    dV1 = 30.303*V0 - 34.848*V1;  
  
    V1 = V1 + dV1*dt;  
    t = t + dt;  
  
    y = [y ; V1];  
end  
  
t = [0:length(y)-1]' * dt;  
  
plot(t,y);  
xlabel('Time (seconds)');  
ylabel('Volts');
```



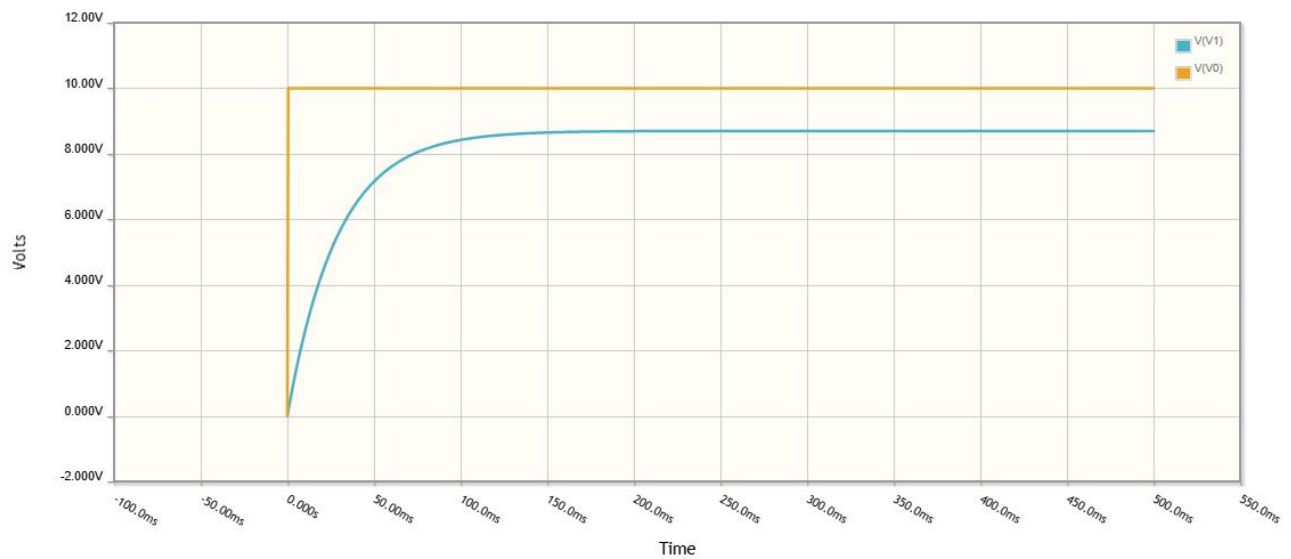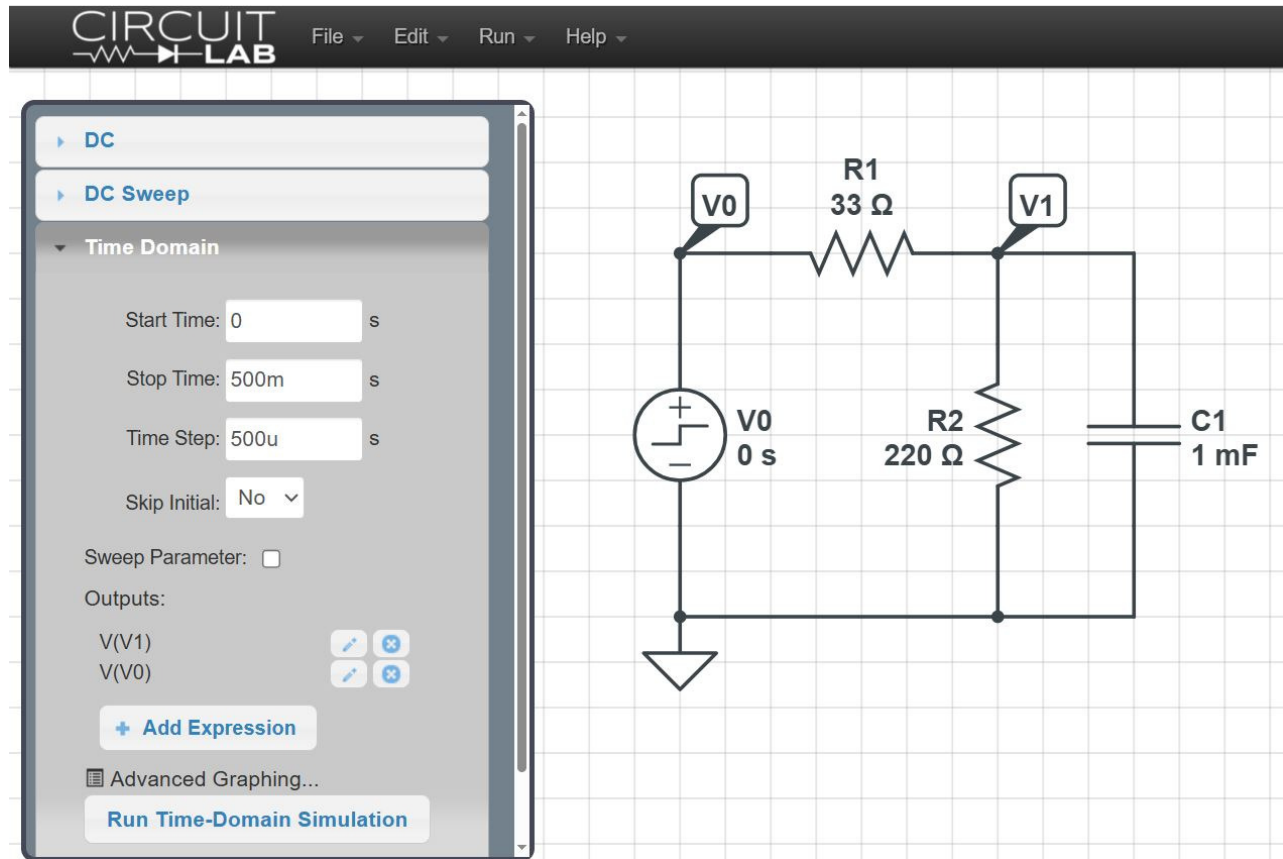
4) Find and plot $V_1(t)$ for 1/2 second using CircuitLab



10-Stage RC Filter

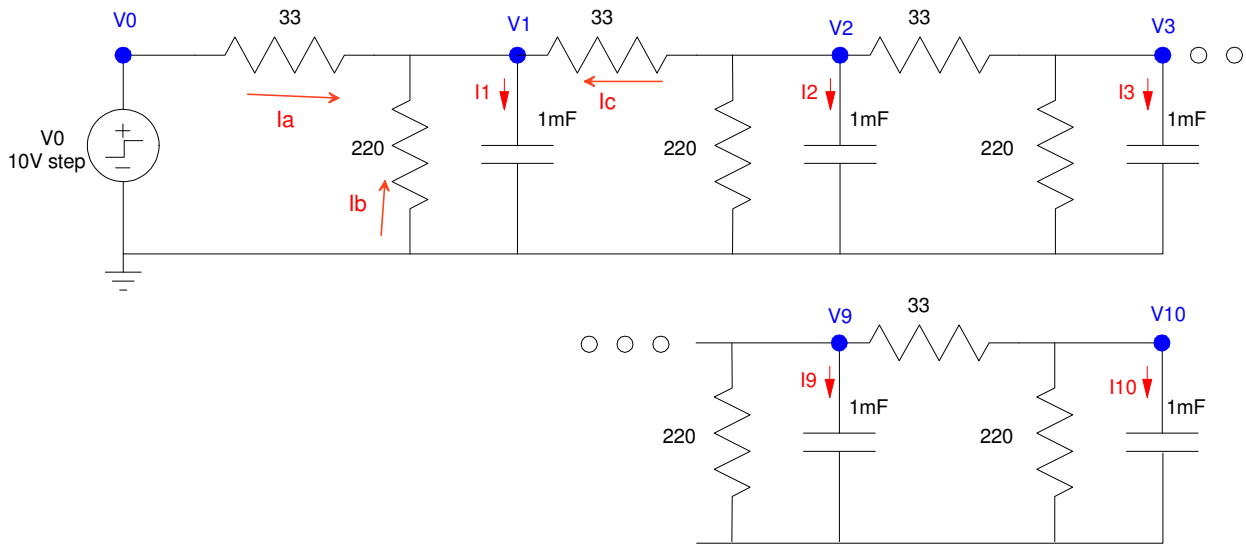5) Write the dynamics for a 10-stage RC filter (repeat for ten stages) as ten coupled differential equations:

$$I_1 = C \frac{dV_1}{dt} = \sum (\text{current to node } V_1)$$



At node V1:

$$I_1 = C \frac{dV_1}{dt} = I_a + I_b + I_c$$

$$I_1 = 0.001 V_1' = \left(\frac{V_0 - V_1}{33} \right) + \left(\frac{0 - V_1}{220} \right) + \left(\frac{V_2 - V_1}{33} \right)$$

Doing some algebra

$$V_1' = 30.3030V_0 - 65.1515V_1 + 30.3030V_2$$

By symmetry, nodes 2..9 are similar

$$V_2' = 30.3030V_1 - 65.1515V_2 + 30.3030V_3$$

⋮

$$V_9' = 30.3030V_8 - 65.1515V_9 + 30.3030V_{10}$$

Node #10 is slightly different since there is no node #11

$$I_{10} = 0.001 V_{10}' = \left(\frac{V_9 - V_{10}}{33} \right) + \left(\frac{0 - V_{10}}{220} \right)$$


$$V_{10}' = 30.3030V_9 - 34.8484V_{10}$$

Forced Response for a 10-Node RC Filter (heat.m):


6) Using Matlab, solve these ten differential equations for $0 < t < 2$ s assuming

- The initial voltages are zero, and
- $V_0 = 10V$.

Resulting voltage vs. node number

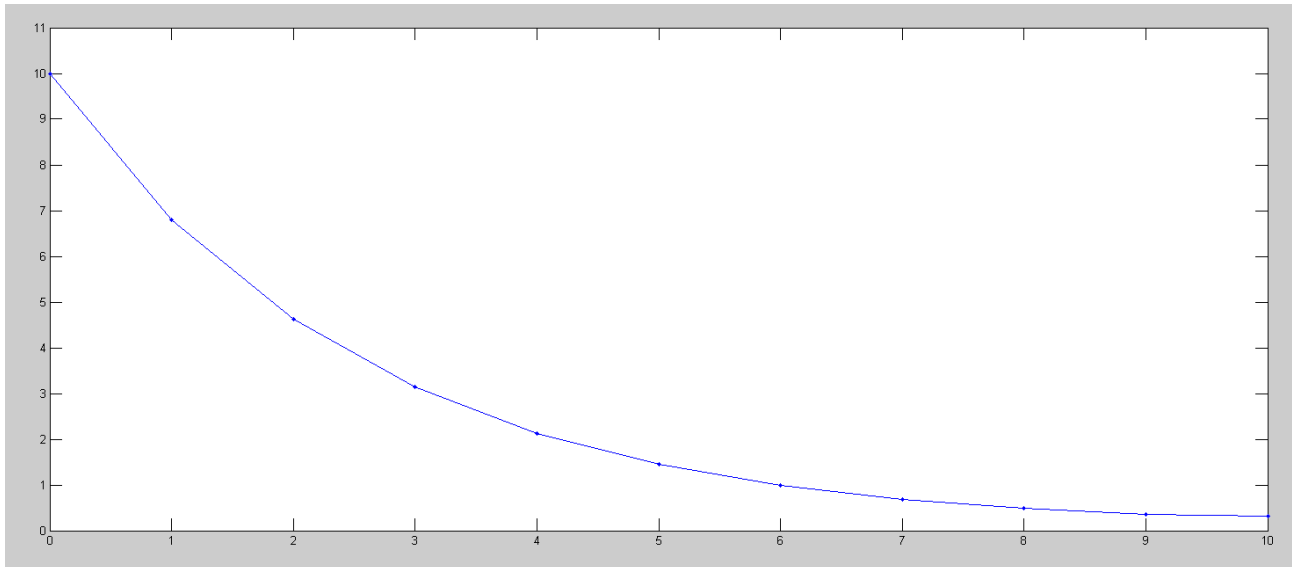

Resulting voltages vs. time

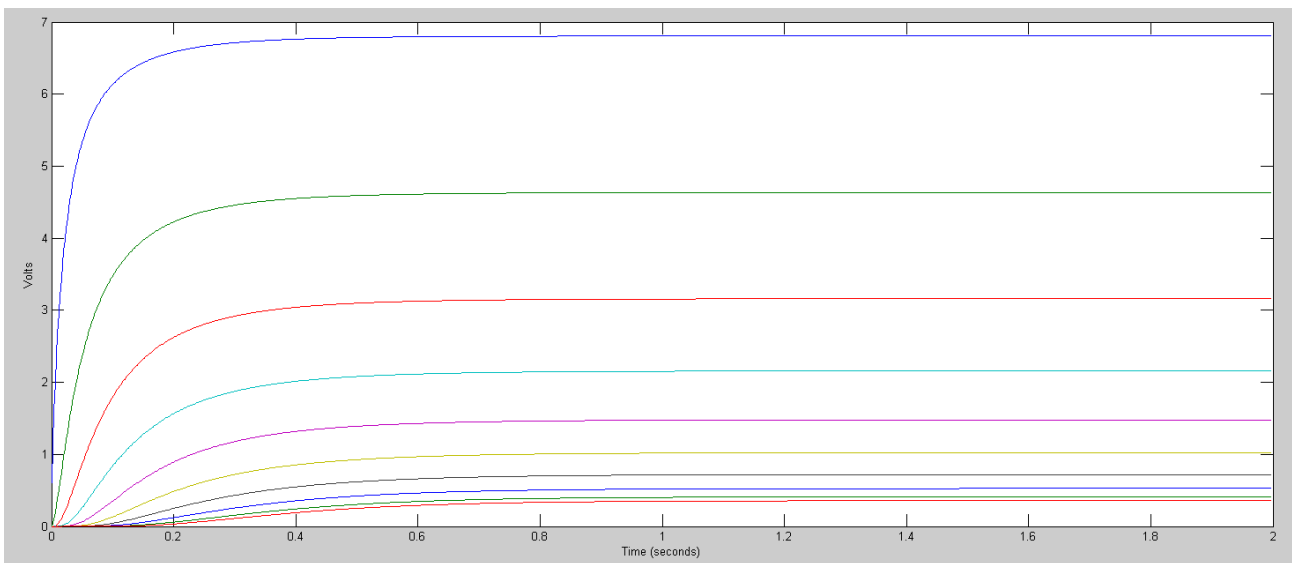

Matlab Code:

```
% 10-stage RC Filter
V = zeros(10,1);
dV = zeros(10,1);
V0 = 10;
dt = 0.002;
t = 0;

y = [];

while(t < 2)

    dV(1) = 30.3030*V0 - 65.1515*V(1) + 30.3030*V(2);
    dV(2) = 30.3030*V(1) - 65.1515*V(2) + 30.3030*V(3);
    dV(3) = 30.3030*V(2) - 65.1515*V(3) + 30.3030*V(4);
    dV(4) = 30.3030*V(3) - 65.1515*V(4) + 30.3030*V(5);
    dV(5) = 30.3030*V(4) - 65.1515*V(5) + 30.3030*V(6);
    dV(6) = 30.3030*V(5) - 65.1515*V(6) + 30.3030*V(7);
    dV(7) = 30.3030*V(6) - 65.1515*V(7) + 30.3030*V(8);
    dV(8) = 30.3030*V(7) - 65.1515*V(8) + 30.3030*V(9);
    dV(9) = 30.3030*V(8) - 65.1515*V(9) + 30.3030*V(10);
    dV(10) = 30.3030*V(9) - 34.8484*V(10);

    V = V + dV*dt;
    t = t + dt;

    y = [y ; V'];

    plot([0:10], [V0;V], '.-');
    ylim([0,11]);
    pause(0.01);


end

t = [0:length(y)-1]' * dt;
plot(t,y);
xlabel('Time (seconds)');
ylabel('Volts');
```

7) Using CircuitLab, find the response of this circuit to a 10V step input. *note: It's OK if you only build this circuit to 3 nodes...*


note: The result is about the same (a little different since only three nodes are simulated)

CircuitLab circuit

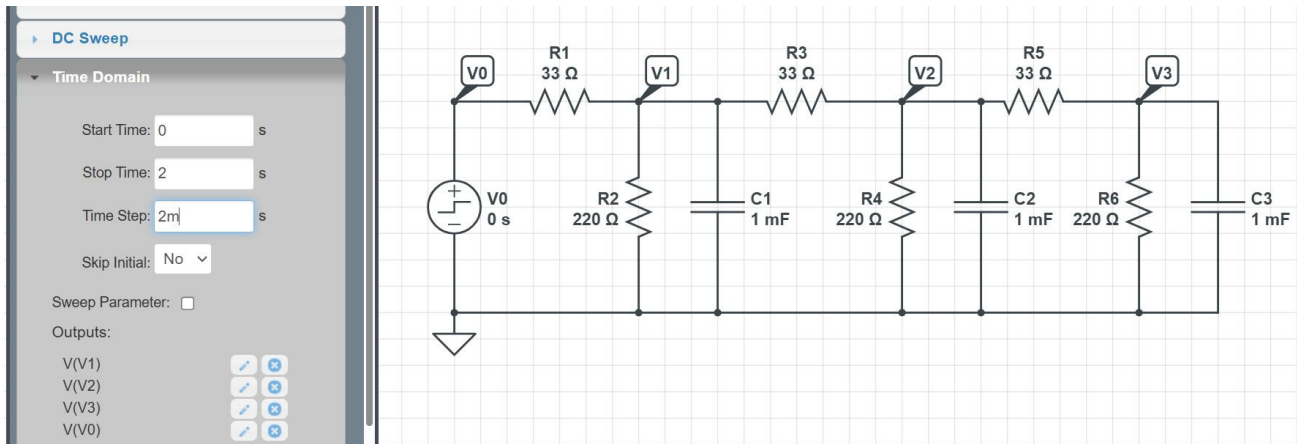

Resulting volages:

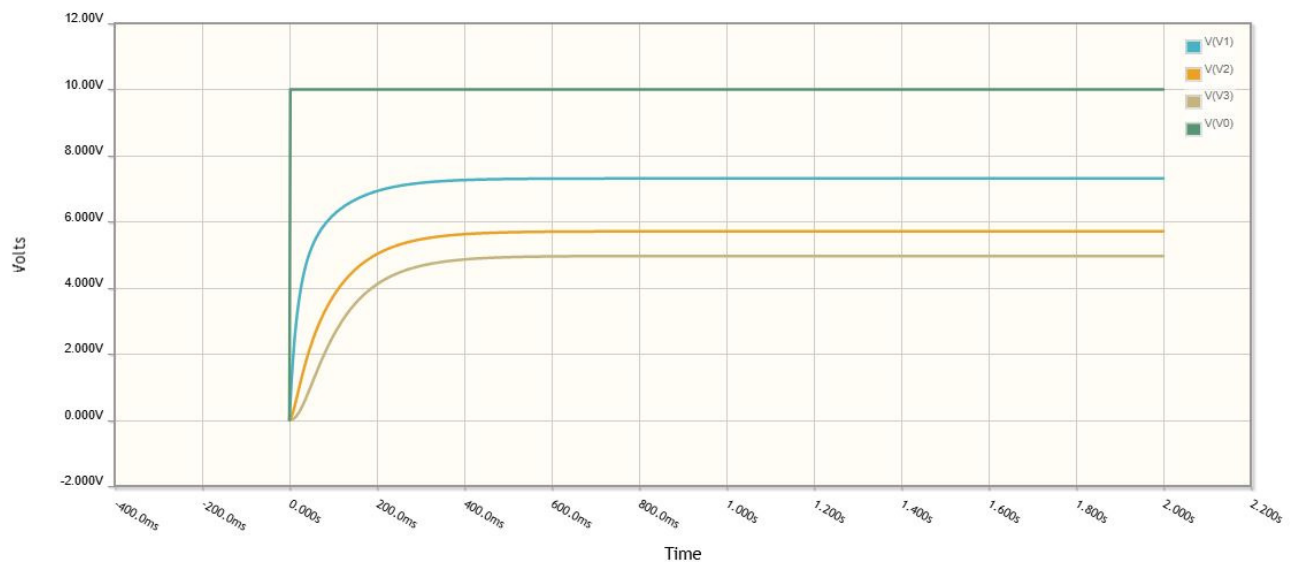- same as computed in Matlab
- CircuitLab uses numerical integration to find the voltages vs. time, same as we did in Matlab



Natural Response: Eigenvectors and Eigenvalues

8) Assume $V_0 = 0V$. Determine the initial conditions of $V_1..V_{10}$ so that

- The maximum voltage is 10V and
- 5a) The voltages go to zero as slow as possible
- 5b) The voltages go to zero as fast as possible.

Simulate the response for these initial conditions in Matlab.

This is an eigenvalue & eigenvector problem. The eigenvectors and eigenvalues can be found using Matlab

First, input the dynamics in matrix form:

$$\frac{dV}{dt} = AV$$

```
>> A = zeros(10,10);
>> for i=1:9
A(i,i) = -65.1515;
A(i+1,i) = 30.3030;
A(i,i+1) = 30.3030;
end
>> A(10,10) = -34.8484;
```

```
-65.1515    30.3030         0         0         0         0         0         0         0         0
 30.3030   -65.1515    30.3030         0         0         0         0         0         0         0
         0    30.3030   -65.1515    30.3030         0         0         0         0         0         0
         0         0    30.3030   -65.1515    30.3030         0         0         0         0         0
         0         0         0    30.3030   -65.1515    30.3030         0         0         0         0
         0         0         0         0    30.3030   -65.1515    30.3030         0         0         0
         0         0         0         0         0    30.3030   -65.1515    30.3030         0         0
         0         0         0         0         0         0    30.3030   -65.1515    30.3030         0
         0         0         0         0         0         0         0    30.3030   -65.1515    30.3030
         0         0         0         0         0         0         0         0    30.3030   -34.8484
```

Find the eigenvalues and eigenvectors using Matlab

```
>> [M,V] = eig(A)
```

M =

fast mode										slow mode
-0.1286	-0.2459	0.3412	0.4063	0.4352	0.4255	0.3780	0.2969	-0.1894		0.0650
0.2459	0.4063	-0.4255	-0.2969	-0.0650	0.1894	0.3780	0.4352	-0.3412		0.1286
-0.3412	-0.4255	0.1894	-0.1894	-0.4255	-0.3412	0.0000	0.3412	-0.4255		0.1894
0.4063	0.2969	0.1894	0.4352	0.1286	-0.3412	-0.3780	0.0650	-0.4255		0.2459
-0.4352	-0.0650	-0.4255	-0.1286	0.4063	0.1894	-0.3780	-0.2459	-0.3412		0.2969
0.4255	-0.1894	0.3412	-0.3412	-0.1894	0.4255	-0.0000	-0.4255	-0.1894		0.3412
-0.3780	0.3780	0.0000	0.3780	-0.3780	0.0000	0.3780	-0.3780	-0.0000		0.3780
0.2969	-0.4352	-0.3412	0.0650	0.2459	-0.4255	0.3780	-0.1286	0.1894		0.4063
-0.1894	0.3412	0.4255	-0.4255	0.3412	-0.1894	0.0000	0.1894	0.3412		0.4255
0.0650	-0.1286	-0.1894	0.2459	-0.2969	0.3412	-0.3780	0.4063	0.4255		0.4352

V =

```
-123.0649 -115.2265 -102.9387 -87.2934 -69.6806 -51.6654 -34.8485 -20.7241 -10.5474 -5.2224
```

The eigenvector is *how* the energy decays


- Something decays slowly as $\exp(-5.22t)$ (the eigenvector in red)
- Something decays quickly as $\exp(-123.06t)$ (the eigenvector in blue)

To simulate the fast eigenvector


- Make the forcing function zero ($V_0 = 0$)
- Make the initial condition the fast eigenvector
- Let the simulation run

The energy decays as $\exp(-123t)$ (very fast)
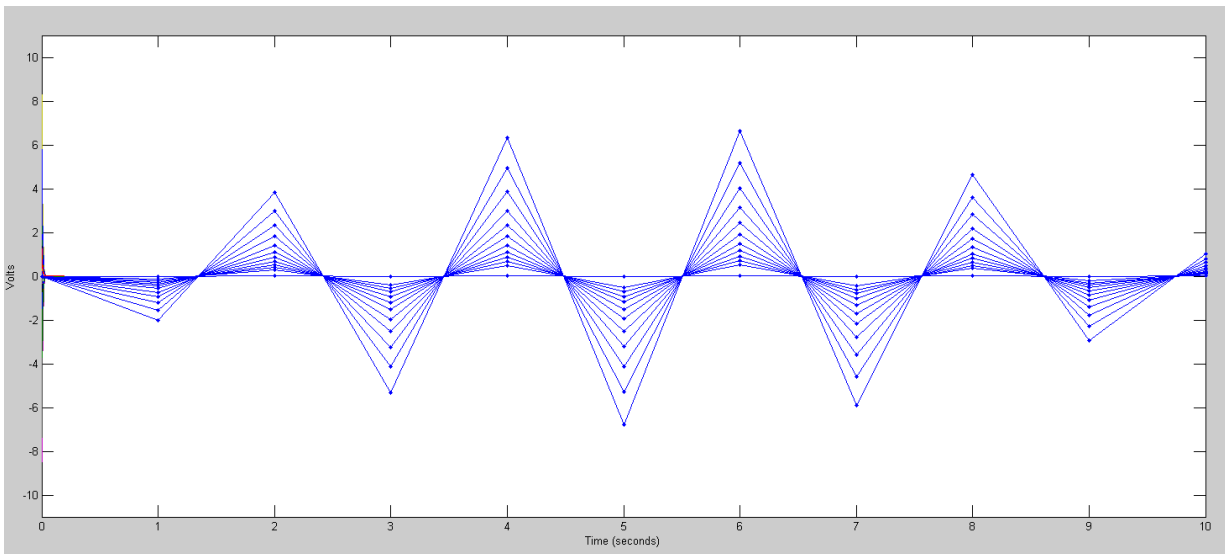
```
V = M(:,1);  
dV = zeros(10,1);  
V0 = 0;  
dt = 0.002;  
t = 0;
```



Fast Mode: Voltages plotted every 2ms

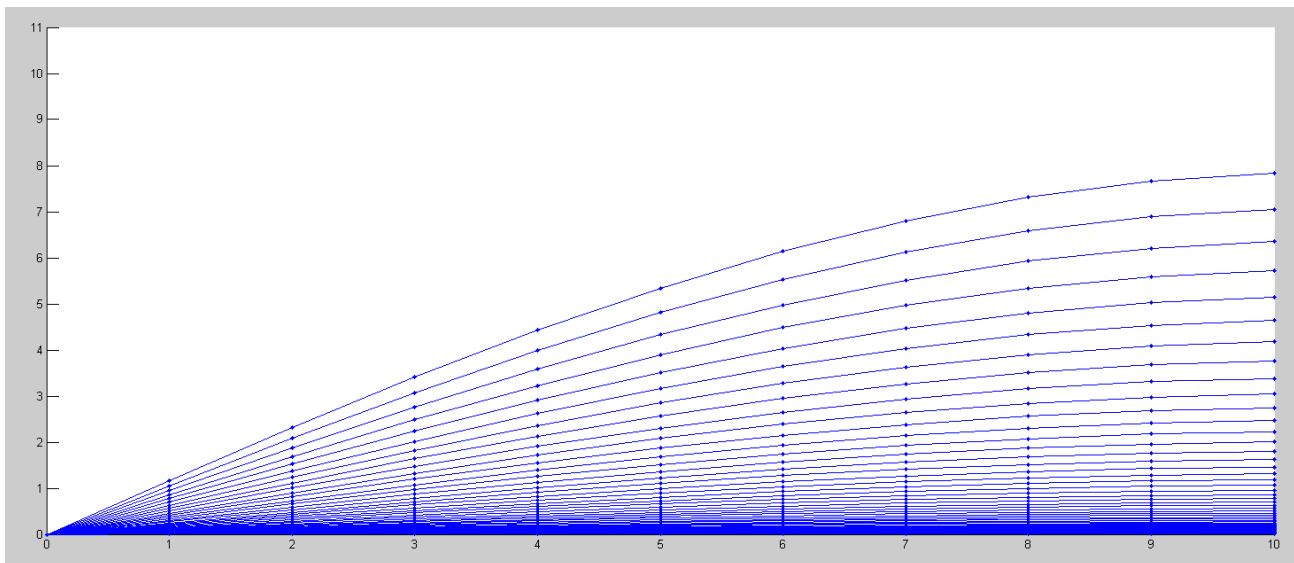

Slow Mode: Voltages plotted every 20ms


9) Assume $V_{in} = 0V$. Pick random voltages for $V_1 \dots V_{10}$ in the range of (0V, 10V):

$V = 10 * \text{rand}(10,1)$

Plot the voltages at $t = 2$. Which eigenvector does it look like?

With a random initial condition, all 10 eigenvectors are excited

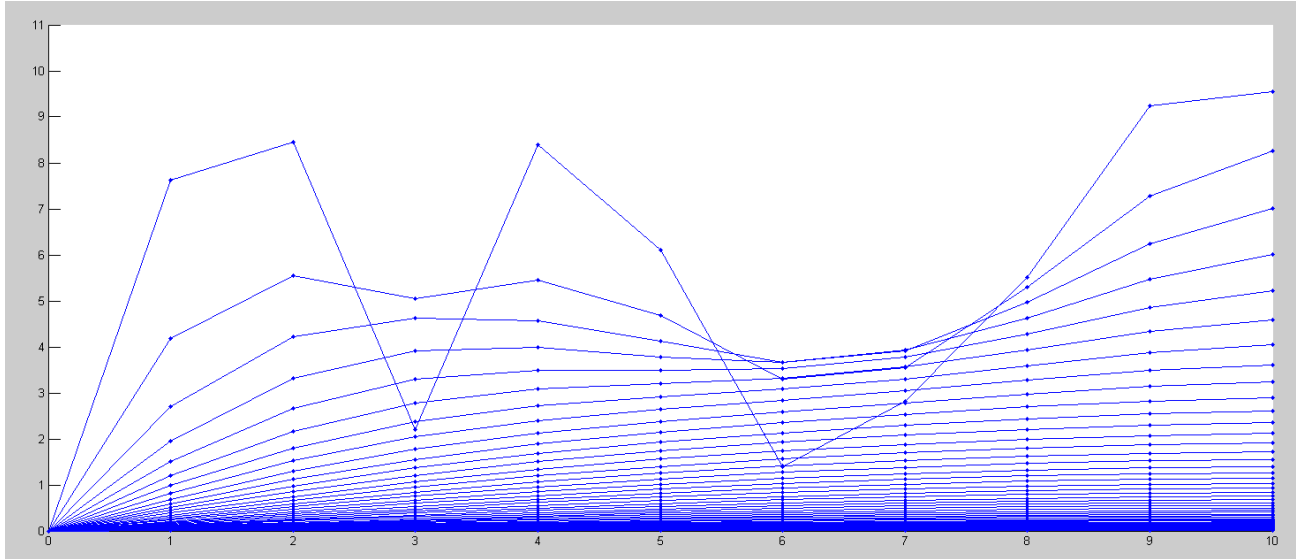- The fast modes decay quickly,
- Leaving the slow mode



Random Initial Condition: Voltages plotted every 20ms