


ECE 111 - Homework #13

ECE 311 Circuits II - Phasors

Phasor Voltages

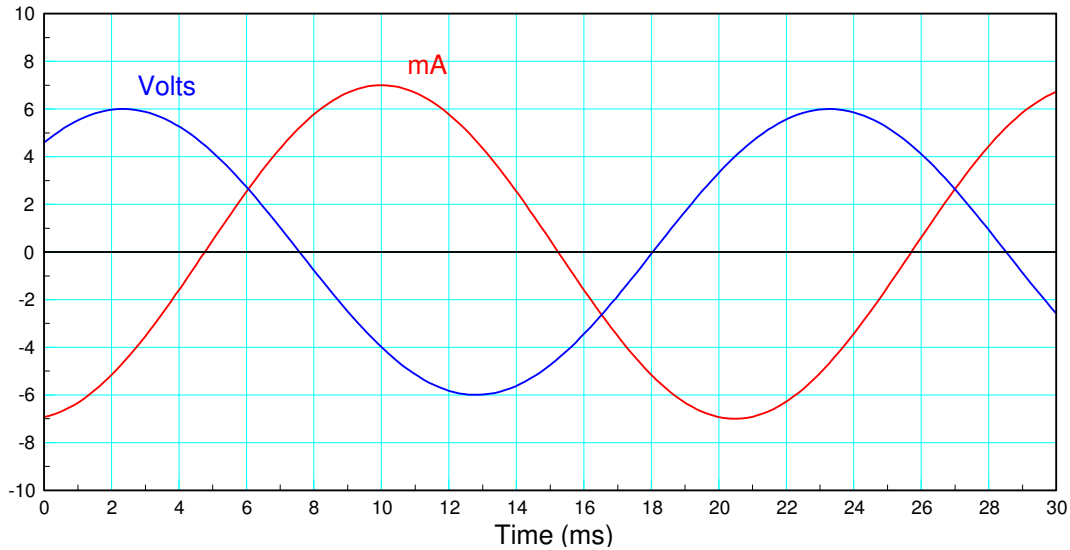1) Express V and I as phasors (i.e. as complex numbers)

- From this, determine the impedance, $Z = V/I$



Polar form is easier with waveforms

- The magnitude is the peak voltage
- The phase is the delay of the peak

Current (red):

- Peak = 7.0mA
- Delay to peak = 10ms
- Period = 21ms
- $\phi = -\left(\frac{10\text{ms}}{21\text{ms}}\right)360^\circ = -171.4^\circ$ $I = 7.0\angle -171.4^\circ \text{ mA}$

Voltage (blue)

- Peak = 6mA
- Delay to peak = 2.2ms
- Period = 21ms (same as voltage)
- $\phi = -\left(\frac{2.2\text{ms}}{21\text{ms}}\right)360^\circ = -37.7^\circ$ $V = 6.0\angle -37.7^\circ \text{ Volts}$

- Impedance

$$Z = \frac{V}{I}$$

$$Z = \left(\frac{6.0 \angle -37.7^\circ V}{7.0 \angle -171.4^\circ mA} \right)$$

$$Z = 857.2 \angle +133.7^\circ$$

or in Matlab

```
>> V = 6*exp(-j*37.7*pi/180)
```

```
V =    4.7473 - 3.6692i
```

```
>> I = 7e-3 * exp(-j*171.4*pi/180)
```


```
I =   -0.0069 - 0.0010i
```

```
>> Z = V / I
```

```
Z = -5.9218e+002 +6.1969e+002i
```

Phasor Impedances

2) Determine the impedance, Z_{ab}

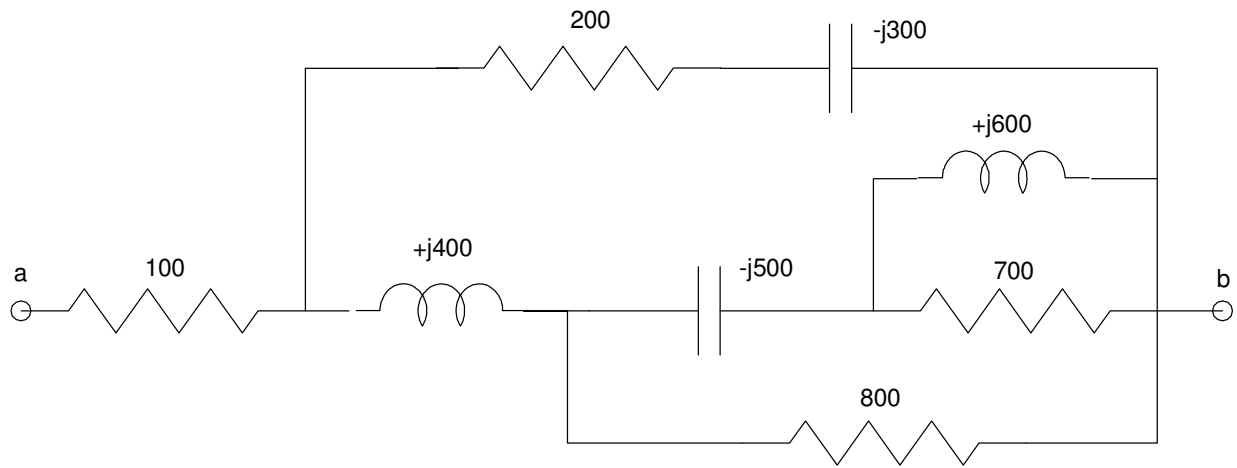

In Matlab

```
>> Z1 = 1 / ( 1/700 + 1/600i)
Z1 = 2.9647e+002 +3.4588e+002i

>> Z2 = Z1 - 500i
Z2 = 2.9647e+002 -1.5412e+002i

>> Z3 = 1 / (1/Z2 + 1/800)
Z3 = 2.2762e+002 -8.0453e+001i


>> Z4 = Z3 + 400i
Z4 = 2.2762e+002 +3.1955e+002i

>> Z5 = 1 / (1/Z4 + 1/(200-300i))
Z5 = 3.2948e+002 -2.5294e+001i


>> Zab = Z5 + 100
Zab = 4.2948e+002 -2.5294e+001i
```

HP42

700	1/x	1/x
1/x	900	200
0	1/x	enter
enter	+	-300
600	1/x	complex
complex		1/x
1/x	0	+
+	enter	1/x
1/x	400	
	complex	100
0	+	+
enter		
-500		
complex		
+		

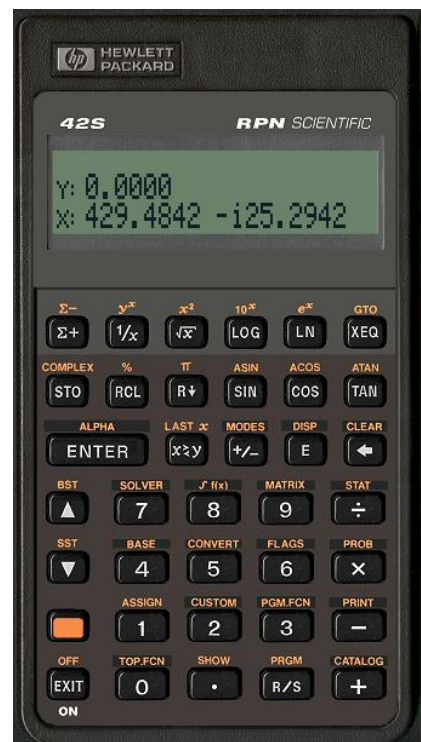

3) Determine the impedance, Z_{ab}

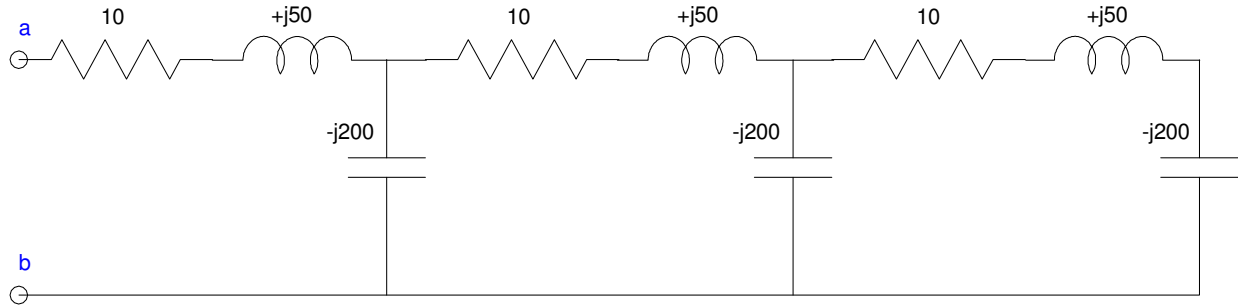

In Matlab

```
>> Z1 = 10 + 50i - 200i
Z1 = 1.0000e+001 -1.5000e+002i

>> Z2 = 1 / (1/Z1 + 1/(-200i))
Z2 = 3.2626 -85.8075i


>> Z3 = Z2 + 10 + 50i
Z3 = 13.2626 -35.8075i

>> Z4 = 1 / (1/Z3 + 1/(-200i))
Z4 = 9.5105 -30.9050i


>> Zab = Z4 + 10 + 50i
Zab = 19.5105 +19.0950i
```

HP42

10	10
enter	enter
50	50
complex	complex
+	+
0	
enter	1/x
-200	0
complex	enter
+	200
	complex
1/x	1/x
0	+
enter	1/x
200	
complex	0
1/x	enter
+	50
1/x	complex
	+

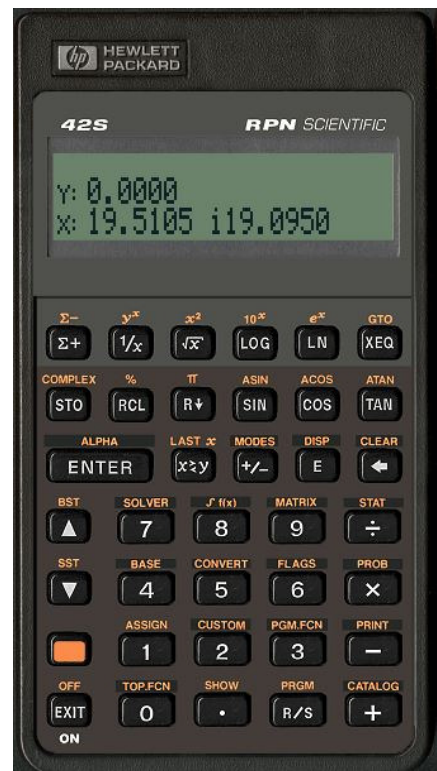

Voltage Nodes with Phasors

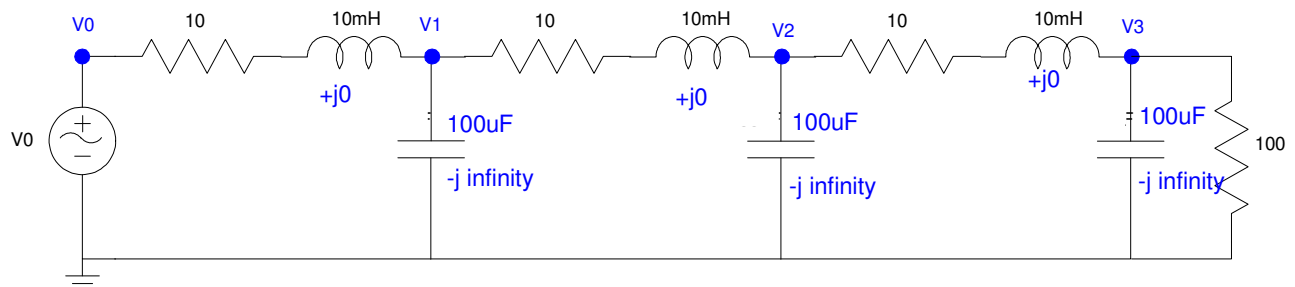

4) Assume $V_0 = 10$.

a) Determine the impedances of each element at 0 rad/sec

$$L \rightarrow j\omega L = j0$$

$$C \rightarrow \frac{1}{j\omega C} = -j\infty$$

b) Write the voltage node equations

$$V_0 = 10$$

$$\left(\frac{V_1 - V_0}{10}\right) + \left(\frac{V_1 - V_2}{10}\right) = 0$$

$$\left(\frac{V_2 - V_1}{10}\right) + \left(\frac{V_2 - V_3}{10}\right) = 0$$

$$\left(\frac{V_3 - V_2}{10}\right) + \left(\frac{V_3}{100}\right) = 0$$

c) Solve for V_1 , V_2 , and V_3 .

Group terms

$$V_0 = 10$$

$$-0.1V_0 + 0.2V_1 - 0.1V_2 = 0$$

$$-0.1V_1 + 0.2V_2 - 0.1V_3 = 0$$

$$-0.1V_2 + 0.11V_3 = 0$$

Place in matrix form

$$\begin{bmatrix} 1 & 0 & 0 & 0 \\ -0.1 & 0.2 & 0.1 & 0 \\ 0 & -0.1 & 0.2 & 0.1 \\ 0 & 0 & -0.1 & 0.11 \end{bmatrix} \begin{bmatrix} V_0 \\ V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} 10 \\ 0 \\ 0 \\ 0 \end{bmatrix}$$

Solve using Matlab

```
>> B = [1,0,0,0;-0.1,0.2,-0.1,0;0,-0.1,0.2,-0.1;0,0,-0.1,0.11]
```

```
    1.0000         0         0         0
   -0.1000    0.2000   -0.1000         0
         0   -0.1000    0.2000   -0.1000
         0         0   -0.1000    0.1100
```

```
>> A = [10;0;0;0]
```


```
    10
     0
     0
     0
```

```
>> V = inv(B)*A
```


```
V0    10.0000
V1     9.2308
V2     8.4615
V3     7.6923
```

5) Check your results in CircuitLab

- The results match

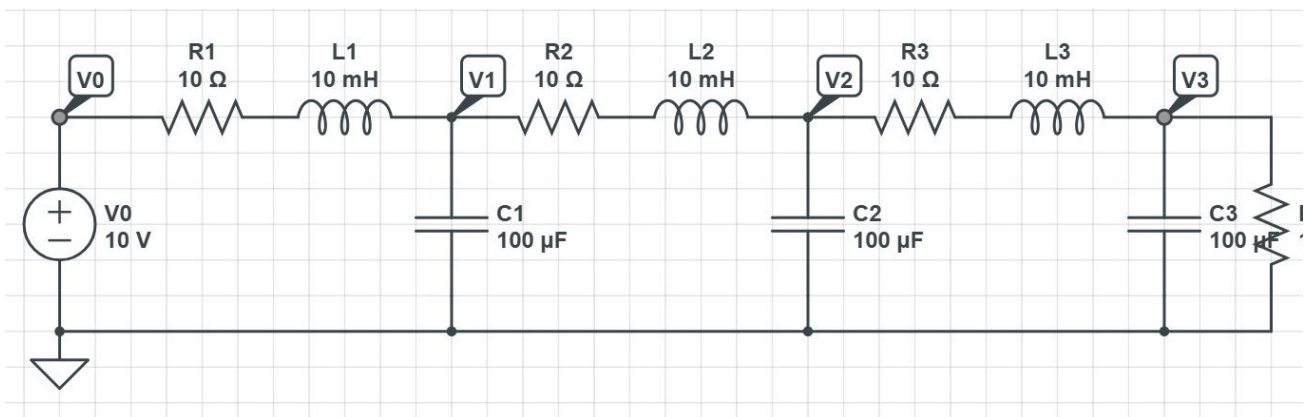

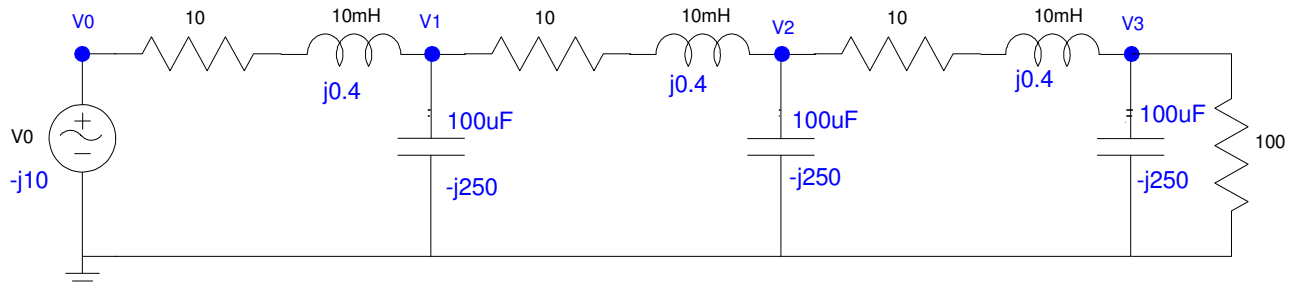6) Assume $V_0 = 10 \sin(40t)$ $10V, 40 \text{ rad/sec sine wave } (6.36\text{Hz})$



a) Determine the impedances of each element at 40 rad/sec

$$V = 0 - j10$$

$$L \rightarrow j\omega L$$

$$= j \cdot 40 \cdot 0.01$$

$$= j0.4$$

$$C \rightarrow \frac{1}{j\omega C}$$

$$= \frac{1}{j \cdot 40 \cdot 100e-6}$$

$$= -j250$$

b) Write the voltage node equations

$$V_0 = -j10$$

$$\left(\frac{V_1 - V_0}{10 + j0.4} \right) + \left(\frac{V_1}{-j250} \right) + \left(\frac{V_1 - V_2}{10 + j0.4} \right) = 0$$

$$\left(\frac{V_2 - V_1}{10 + j0.4} \right) + \left(\frac{V_2}{-j250} \right) + \left(\frac{V_2 - V_3}{10 + j0.4} \right) = 0$$

$$\left(\frac{V_3 - V_2}{10 + j0.4} \right) + \left(\frac{V_3}{100} \right) = 0$$

c) Solve for V1, V2, and V3 as complex numbers

Group terms and simplify

$$V_0 = -j10$$

$$-\left(\frac{1}{10+j0.4}\right)V_0 + \left(\left(\frac{1}{10+j0.4}\right) + \left(\frac{1}{-j250}\right) + \left(\frac{1}{10+j0.4}\right)\right)V_1 - \left(\frac{1}{10+j0.4}\right)V_2 = 0$$

$$-\left(\frac{1}{10+j0.4}\right)V_1 + \left(\left(\frac{1}{10+j0.4}\right) + \left(\frac{1}{-j250}\right) + \left(\frac{1}{10+j0.4}\right)\right)V_2 - \left(\frac{1}{10+j0.4}\right)V_3 = 0$$

$$-\left(\frac{1}{10+j0.4}\right)V_2 + \left(\left(\frac{1}{10+j0.4}\right) + \left(\frac{1}{-j250}\right)\right)V_3 = 0$$

Place in matrix form

$$\begin{bmatrix} 1 & 0 & 0 & 0 \\ \left(\frac{-1}{10+j0.4}\right) & \left(\left(\frac{2}{10+j0.4}\right) + \left(\frac{1}{-j250}\right)\right) & \left(\frac{-1}{10+j0.4}\right) & 0 \\ 0 & \left(\frac{-1}{10+j0.4}\right) & \left(\left(\frac{2}{10+j0.4}\right) + \left(\frac{1}{-j250}\right)\right) & \left(\frac{-1}{10+j0.4}\right) \\ 0 & 0 & \left(\frac{-1}{10+j0.4}\right) & \left(\left(\frac{1}{10+j0.4}\right) + \left(\frac{1}{-j250}\right)\right) \end{bmatrix} \begin{bmatrix} V_0 \\ V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} -j10 \\ 0 \\ 0 \\ 0 \end{bmatrix}$$

Solve using Matlab

```
a1 = [1,0,0,0];
a2 = [-1/(10+0.4j), 2/(10+0.4j)+1/(-250j), -1/(10+0.4j), 0];
a3 = [0, -1/(10+0.4j), 2/(10+0.4j)+1/(-250j), -1/(10+0.4j)];
a4 = [0,0,-1/(10+0.4j), 1/(10+0.4j)+1/(-250j)];
A = [a1;a2;a3;a4]
```

```
>> B = [-10i;0;0;0];
```

```
V = inv(A)*B
```

```
V0      0 -10.0000i
V1  -1.1737 - 9.8279i
V2  -1.9524 - 9.6871i
V3  -2.3405 - 9.6088i
```

meaning

```
V0 = 10 sin(40t)
V1  -1.1737 cos(40t) + 9.8279 sin(40t)
V2  -1.9524 cos(40t) + 9.68761 sin(40t)
V3  -2.3405 cos(40t) + 9.6088 sin(40t)
```

In polar form, the magnitude is

```
>> abs(V)
```

```
V0  10.0000
V1   9.8978
V2   9.8819
V3   9.8898
```

The phase shift in degrees is

```
>> angle(V)*180/pi
```

```
-90.0000  
-96.8103  
-101.3952  
-103.6894
```

7) Check your results in CircuitLab using a transient simulation for 500ms (time step = 5us).

Use a sinusoidal source for V0


- Amplitude = 10 Volts
- Frequency = 6.3662Hz

$$\omega = 2\pi f$$

$$f = \frac{40}{2\pi} = 6.3622 \text{ Hz}$$

- Delay = 0 degrees (CircuitLab uses sine waves rather than cosine waves)

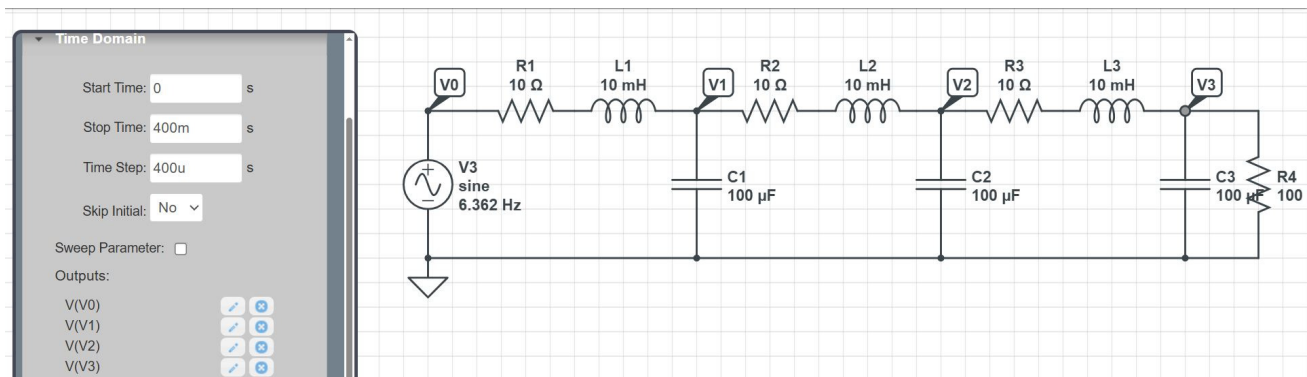Run a time-domain simulation for a couple cycles



This shows the waveforms

- Amplitudes match calculations
- Phase shift (delays) match calculations
- AC circuit analysis is just like DC analysis, only you're using complex numbers

