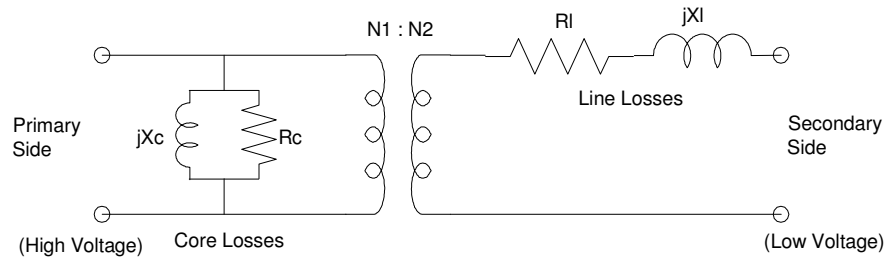


ECE 111: Homework 16

ECE 331 Energy Conversion

1) Determine the circuit model for a 13.2kV : 240V transformer is tested with the following test results:



Transformer Model

	V	Power	pf
Open-Circuit Test	V1 = 9.6kV	15 W	0.015
Short-Circuit Test	V2 = 20V	10 W	0.99

Open Circuit Test (R_c and jX_c)

$$P = V \cdot I \cdot pf$$

$$15W = 9.6kV \cdot I \cdot 0.015$$

$$I = 0.1042A$$

$$Z = \left(\frac{V}{I} \right) \angle \arccos(pf)$$

$$Z = \left(\frac{9600V}{0.1042A} \right) \angle \arccos(0.015)$$

$$Z = 1382.4 + j92,150$$

This is the series model. To get the parallel model, take the inverse

$$\frac{1}{Z} = \frac{1}{R_c} + \frac{1}{jX_c}$$

In Matlab

```
>> V = 9600;
>> I = 15 / (9600*0.015)
```

```
I = 0.1042
```

```

>> Z = V/I * exp(j*acos(0.015))
Z = 1.3824e+003 +9.2150e+004i
>> 1/Z
ans = 1.6276e-007 -1.0849e-005i
>> Rc = 1 / real(1/Z)
Rc = 6.1440e+006
>> Xc = -1 / imag(1/Z)
Xc = 9.2170e+004

```

Short Circuit Test: This gives you RL and jXL


```

>> V = 20;
>> I = 10 / (20*0.99)
I = 0.5051
>> Z = V/I * exp(j*acos(0.99))
RL      jXL
Z = 39.2040 + 5.5863i

```

For the utility grid on the back of the page....

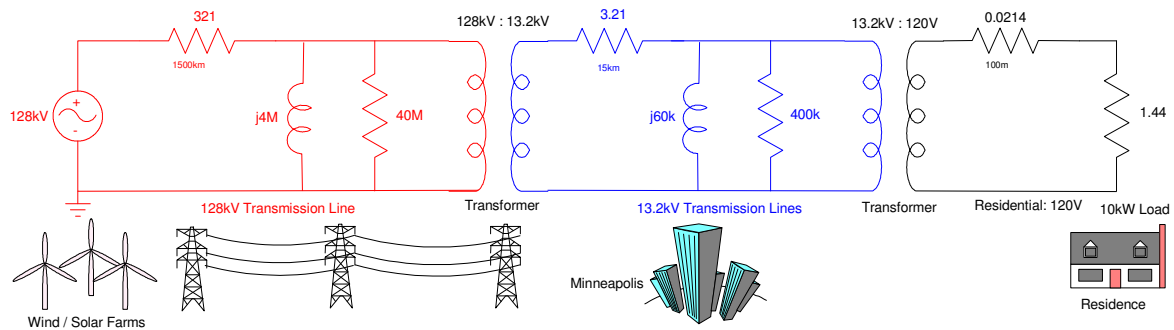2) Convert the voltages and impeances to the 120V node (right side)



Impedances convert as the turn-ratio squared

```
>> V0 = 120;
>> R01 = 321 * (120/128000)^2

R01 = 2.8213e-004

>> R1 = 40e6 * (120/128000)^2

R1 = 35.1563

>> X1 = j*4e6 * (120/128000)^2

X1 = 0 + 3.5156i

>> R12 = 3.21*(120/13200)^2

R12 = 2.6529e-004

>> R2 = 400e3 * (120/13200)^2


R2 = 33.0579

>> X2 = j*60e3 * (120/13200)^2

X2 = 0 + 4.9587i

>> R23 = 0.0214;
>> R3 = 1.44;
>>
```

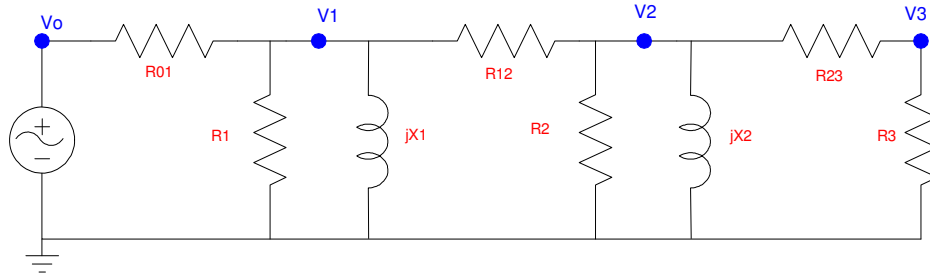3) Write the voltage node equations for this circuit (with transformers removed)



$$V_0 = 120$$

$$\left(\frac{V_1 - V_0}{R_{01}} \right) + \left(\frac{V_1}{R_1} \right) + \left(\frac{V_1}{jX_1} \right) + \left(\frac{V_1 - V_2}{R_{12}} \right) = 0$$

$$\left(\frac{V_2 - V_1}{R_{12}} \right) + \left(\frac{V_2}{R_2} \right) + \left(\frac{V_2}{jX_2} \right) + \left(\frac{V_2 - V_3}{R_{23}} \right) = 0$$

$$\left(\frac{V_3 - V_2}{R_{23}} \right) + \left(\frac{V_3}{R_3} \right)$$

4) Determine the voltages at each node

Group terms

$$V_0 = 120$$

$$-\left(\frac{1}{R_{01}} \right) V_0 + \left(\frac{1}{R_{01}} + \frac{1}{R_1} + \frac{1}{jX_1} + \frac{1}{R_{12}} \right) V_1 - \left(\frac{1}{R_{12}} \right) V_2 = 0$$

$$-\left(\frac{1}{R_{12}} \right) V_1 + \left(\frac{1}{R_{12}} + \frac{1}{R_2} + \frac{1}{jX_2} + \frac{1}{R_{23}} \right) V_2 - \left(\frac{1}{R_{23}} \right) V_3 = 0$$

$$-\left(\frac{1}{R_{23}} \right) V_2 + \left(\frac{1}{R_{23}} + \frac{1}{R_3} \right) V_3 = 0$$

Place in matrix form

$$\begin{bmatrix} 1 & 0 & 0 & 0 \\ \left(\frac{-1}{R_{01}} \right) & \left(\frac{1}{R_{01}} + \frac{1}{R_1} + \frac{1}{jX_1} + \frac{1}{R_{12}} \right) & \left(\frac{-1}{R_{12}} \right) & 0 \\ 0 & \left(\frac{-1}{R_{12}} \right) & \left(\frac{1}{R_{12}} + \frac{1}{R_2} + \frac{1}{jX_2} + \frac{1}{R_{23}} \right) & \left(\frac{-1}{R_{23}} \right) \\ 0 & 0 & \left(\frac{-1}{R_{23}} \right) & \left(\frac{1}{R_{23}} + \frac{1}{R_3} \right) \end{bmatrix} \begin{bmatrix} V_0 \\ V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} 120 \\ 0 \\ 0 \\ 0 \end{bmatrix}$$

Solve using Matlab

```

V0 = 120;
R01 = 321 * (120/128000)^2;
R1 = 40e6 * (120/128000)^2;
X1 = j*4e6 * (120/128000)^2;
R12 = 3.21*(120/13200)^2;
R2 = 400e3 * (120/13200)^2;
X2 = j*60e3 * (120/13200)^2;
R23 = 0.0214;
R3 = 1.44;

b1 = [1,0,0,0];
b2 = [-1/R01, 1/R01+1/R1+1/X1+1/R12, -1/R12, 0];
b3 = [0, -1/R12, 1/R12+1/R2+1/X2+1/R23, -1/R23];
b4 = [0,0,-1/R23, 1/R23+1/R3];
B = [b1;b2;b3;b4];
A = [120;0;0;0];
V = inv(B)*A

V0 120.00
V1 119.97 + 0.02i
V2 119.95 + 0.02i
V3 118.20 + 0.02i

```

Determine the efficiency of this system

- Ignoring the core losses
 - Assumes a large number of customers share these losses
- Including the core losses
 - Assumes a single customer

In Matlab

```

V0 = V(1);
V1 = V(2);
V2 = V(3);
V3 = V(4);

P01 = (abs(V0-V1))^2 / R01
P12 = (abs(V1-V2))^2 / R12
P23 = (abs(V2-V3))^2 / R23
P1 = (abs(V1))^2 / R1
P2 = (abs(V2))^2 / R2
P3 = (abs(V3))^2 / R3

eff1 = P3 / (P1 + P2 + P3 + P01 + P12 + P23)
eff2 = P3 / (P3 + P01 + P12 + P23)

P01 = 3.2002
P12 = 2.1041
P23 = 144.1755
P1 = 409.4284
P2 = 435.2524
P3 = 9.7015e+003

```

eff1 = 0.9071

eff2 = 0.9848

If you include everything, the power grid is 90.71% efficient

- If there is only one customer, 90.71% of the power generated gets to the customer

If you ignore the core losses, the power grid is 98.48% efficient

- If there are many customers (so the core losses are distributed across many accounts), the power grid is 98.48% efficient.

An AC power grid using Tesla's model is quite efficient. This only works for AC signals, however (which is why our power grid is 60Hz rather than Edison's DC power grid).

