


ECE 111 - Homework #13

ECE 311 Circuits II - Phasors
Due Monday, April 21st. Please submit via email or on BlackBoard

Phasor Voltages

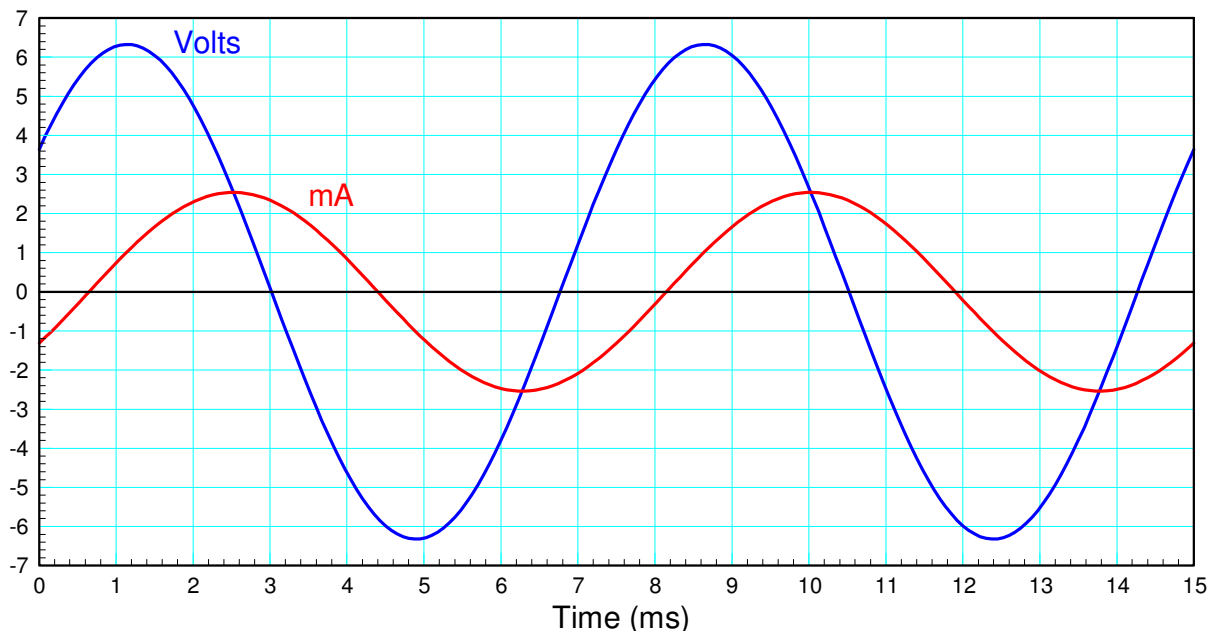1) Express V and I as phasors (i.e. as complex numbers)

- From this, determine the impedance, $Z = V/I$



Voltage:

- Peak = 6.2
- Delay = 1.2ms
- Period = 7.5ms

$$\theta = -\left(\frac{1.2\text{ms}}{7.5\text{ms}}\right) 360^\circ = -57.6^\circ$$

$$V = 6.2 \angle -57.6^\circ \text{ Volts}$$

Current

- Peak = 2.5mA
- Delay = 2.5ms
- Period = 7.5ms

$$\theta = -\left(\frac{2.5\text{ms}}{7.5\text{ms}}\right) 360^\circ = -120^\circ$$

$$I = 2.5 \angle -120^\circ \text{ mA}$$

The impedance is then

$$Z = \frac{V}{I}$$

$$Z = \left(\frac{8.2 \angle -57.6^\circ}{0.0025 \angle -120^\circ} \right)$$


$$Z = 3280 \angle 62.4^\circ$$

or if you prefer rectangular form


$$Z = 1519.61 + j290.67$$

Phasor Impedances

2) Determine the impedance, Z_{ab}

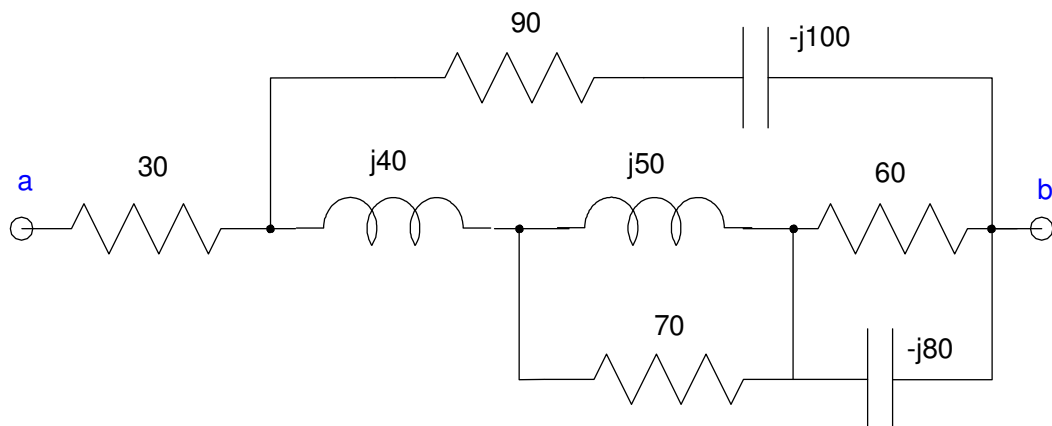

3) Determine the impedance, Z_{ab}

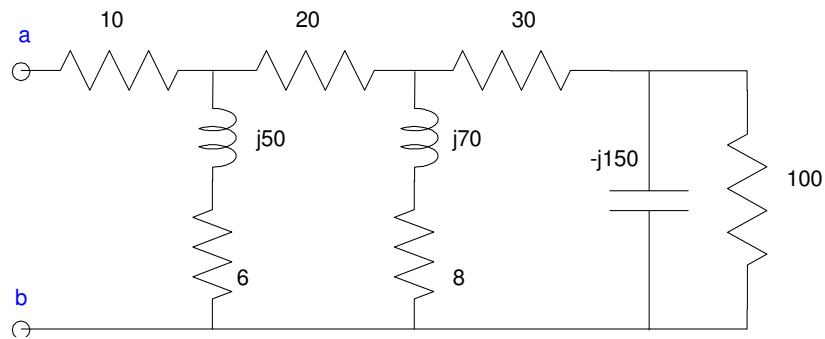

In Matlab

```
>> Za = 1 / (1/100+ 1/(-150i))
Za = 69.2308 -46.1538i

>> Zb = Za + 30
Zb = 99.2308 -46.1538i

>> Zc = 1 / ( 1/Zb + 1/(8+70i) )
Zc = 48.7605 +50.4908i

>> Zd = 20 + Zc
Zd = 68.7605 +50.4908i


>> Ze = 1 / ( 1/Zd + 1/(6+50i) )
Ze = 13.8990 +31.3568i

>> Zab = Ze + 10
Zab = 23.8990 +31.3568i
```

On an HP Prime

```
100
1/x
0-150i
1/x
+
1/x
30
+
1/x
8+70i
1/x
+
1/x
20
+
1/x
6+50i
1/x
+
1/x
10
+
```

Voltage Nodes with Phasors

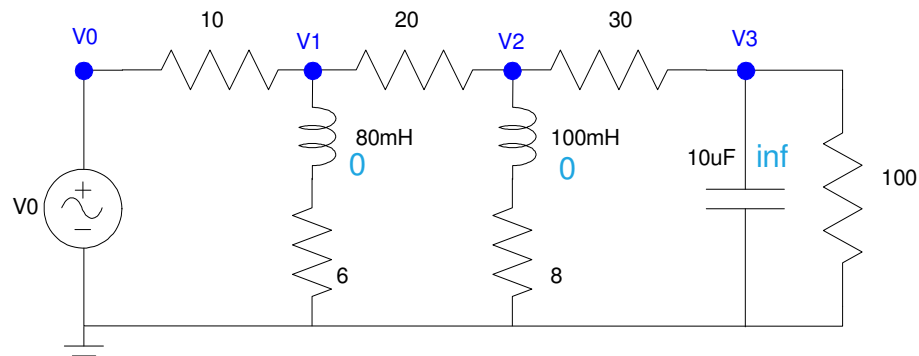

4) Assume $V_0 = 10$.

a) Determine the impedances of each element at 0 rad/sec

- Inductors are zero Ohms at DC
- Capacitors are infinite Ohms at DC

b) Write the voltage node equations

$$V_0 = 10$$

$$\left(\frac{V_1 - V_0}{10} \right) + \left(\frac{V_1}{6} \right) + \left(\frac{V_1 - V_2}{20} \right) = 0$$

$$\left(\frac{V_2 - V_1}{20} \right) + \left(\frac{V_2}{8} \right) + \left(\frac{V_2 - V_3}{30} \right) = 0$$

$$\left(\frac{V_3 - V_2}{30} \right) + \left(\frac{V_3}{\infty} \right) + \left(\frac{V_3}{100} \right) = 0$$

you can leave out the term that divides by infinity. This current is zero.

c) Solve for V_1 , V_2 , and V_3 .

Group terms

$$V_0 = 10$$

$$-\left(\frac{1}{10} \right) V_0 + \left(\frac{1}{10} + \frac{1}{6} + \frac{1}{20} \right) V_1 - \left(\frac{1}{20} \right) V_2 = 0$$

$$-\left(\frac{1}{20} \right) V_1 + \left(\frac{1}{20} + \frac{1}{8} + \frac{1}{30} \right) V_2 - \left(\frac{1}{30} \right) V_3 = 0$$

$$-\left(\frac{1}{30} \right) V_2 + \left(\frac{1}{30} + \frac{1}{100} \right) V_3 = 0$$

Place in matrix form

$$\begin{bmatrix} 1 & 0 & 0 & 0 \\ \left(\frac{-1}{10}\right) & \left(\frac{1}{10} + \frac{1}{6} + \frac{1}{20}\right) & \left(\frac{-1}{20}\right) & 0 \\ 0 & \left(\frac{-1}{20}\right) & \left(\frac{1}{20} + \frac{1}{8} + \frac{1}{30}\right) & \left(\frac{-1}{30}\right) \\ 0 & 0 & \left(\frac{-1}{30}\right) & \left(\frac{1}{30} + \frac{1}{100}\right) \end{bmatrix} \begin{bmatrix} V_0 \\ V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} 10 \\ 0 \\ 0 \\ 0 \end{bmatrix}$$

Solve using Matlab

```
>> a1= [1,0,0,0];
>> a2 = [-1/10, 1/10+1/6+1/20,-1/20,0];
>> a3 = [0,-1/20,1/20+1/8+1/30,-1/30];
>> a4 = [0,0,-1/30,1/30+1/100];
>> A = [a1;a2;a3;a4]
```

```
    1.0000         0         0         0
   -0.1000    0.3167   -0.0500         0
         0   -0.0500    0.2083   -0.0333
         0         0   -0.0333    0.0433
```


```
>> B = [10;0;0;0]
```

```
    10
     0
     0
     0
```

```
>> V = inv(A)*B
```

```
v0    10.0000
v1     3.3005
v2     0.9033
v3     0.6948
```

5) Check your results in CircuitLab

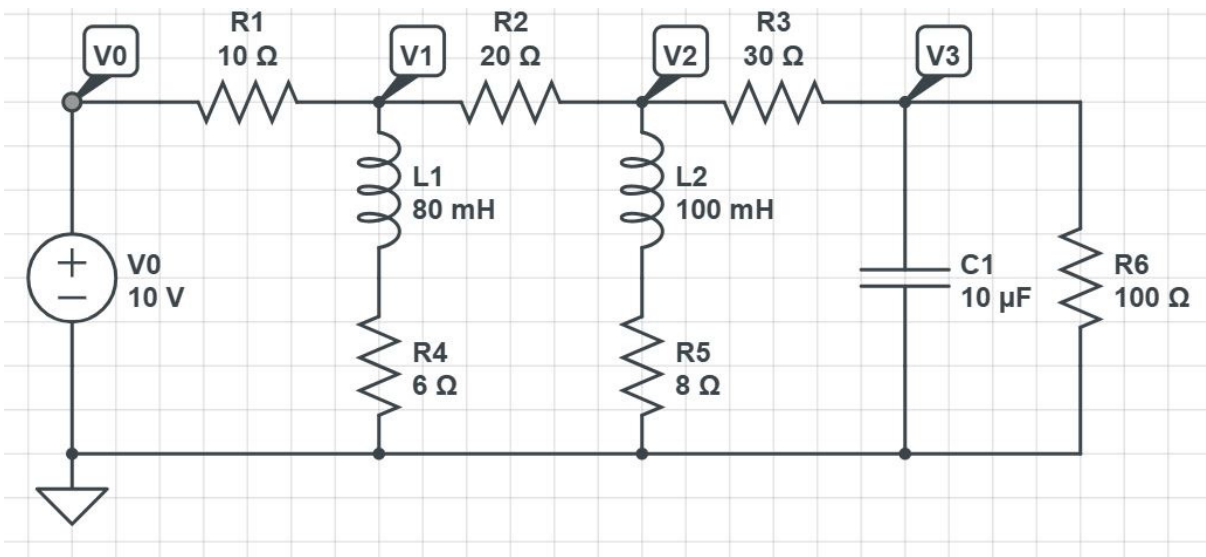

DC	
V(V0)	10.00 V
V(V1)	3.301 V
V(V2)	903.3 mV
V(V3)	694.8 mV
+ Add Expression	


This matches previous calculations

```
>> V = inv(A) * B
```

V0	10.0000
V1	3.3005
V2	0.9033
V3	0.6948

6) Assume $V_0 = 10 \sin(628t)$

10V, 628 rad/sec sine wave (100Hz)

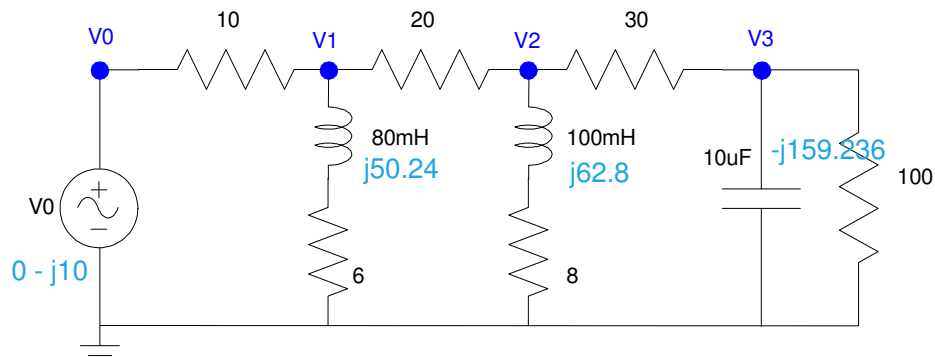

a) Determine the impedances of each element at 628 rad/sec

80mH:

$$Z = j\omega L = j \cdot 628 \cdot 0.08$$

$$Z = j50.24\Omega$$

100mH

$$Z = j\omega L = j62.8\Omega$$

10uF

$$Z = \frac{1}{j\omega C} = -j159.236\Omega$$

V0

$$V = 0 - j10$$

real = cosine

-imag = sine

b) Write the voltage node equations

same as we had at DC, only now with complex numbers

$$V_0 = 0 - j10$$

$$\left(\frac{V_1 - V_0}{10} \right) + \left(\frac{V_1}{6 + j50.24} \right) + \left(\frac{V_1 - V_2}{20} \right) = 0$$

$$\left(\frac{V_2 - V_1}{20} \right) + \left(\frac{V_2}{8 + j62.8} \right) + \left(\frac{V_2 - V_3}{30} \right) = 0$$

$$\left(\frac{V_3 - V_2}{30} \right) + \left(\frac{V_3}{-j159.236} \right) + \left(\frac{V_3}{100} \right) = 0$$

c) Solve for V1, V2, and V3 as complex numbers

Group terms

$$V_0 = -j10$$

$$-\left(\frac{1}{10}\right)V_0 + \left(\frac{1}{10} + \frac{1}{6+j50.24} + \frac{1}{20}\right)V_1 - \left(\frac{1}{20}\right)V_2 = 0$$

$$-\left(\frac{1}{20}\right)V_1 + \left(\frac{1}{20} + \frac{1}{8+j62.8} + \frac{1}{30}\right)V_2 - \left(\frac{1}{30}\right)V_3 = 0$$

$$-\left(\frac{1}{30}\right)V_2 + \left(\frac{1}{30} + \frac{1}{100} + \frac{1}{-j159.236}\right)V_3 = 0$$

Place in matrix form

$$\begin{bmatrix} 1 & 0 & 0 & 0 \\ \left(\frac{-1}{10}\right) & \left(\frac{1}{10} + \frac{1}{6+j50.24} + \frac{1}{20}\right) & \left(\frac{-1}{20}\right) & 0 \\ 0 & \left(\frac{-1}{20}\right) & \left(\frac{1}{20} + \frac{1}{8+j62.8} + \frac{1}{30}\right) & \left(\frac{-1}{30}\right) \\ 0 & 0 & \left(\frac{-1}{30}\right) & \left(\frac{1}{30} + \frac{1}{100} + \frac{1}{-j159.236}\right) \end{bmatrix} \begin{bmatrix} V_0 \\ V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} -j10 \\ 0 \\ 0 \\ 0 \end{bmatrix}$$

Solve using Matlab

```
a1= [1,0,0,0];
a2 = [-1/10, 1/10+1/(6+50.24i)+1/20,-1/20,0];
a3 = [0,-1/20,1/20+1/(8+62.8i)+1/30,-1/30];
a4 = [0,0,-1/30,1/30+1/100+1/(-159.236i)];
A = [a1;a2;a3;a4]
```

```
1.0000      0      0      0
-0.1000      0.1523 - 0.0196i -0.0500      0
      0      -0.0500      0.0853 - 0.0157i -0.0333
      0      0      -0.0333      0.0433 + 0.0063i
```

```
>> B = [-10i;0;0;0]
```

```
      0 -10.0000i
      0
      0
      0
```

```
>> V = inv(A)*B
```

```
V0      0 -10.0000i
V1      2.0597 - 8.3895i
V2      2.9829 - 6.3703i
V3      1.5518 - 5.1251i
```

d) Express V1, V2, and V3 in terms of sine and cosine function:

```
V0 =      0 cos(628t) + 10.0000 sin(628t)
V1 =      2.0597 cos(628t) +      8.3895 sin(628t)
V2 =      2.9829 cos(628t) +      6.3703 sin(628t)
V3 =      1.5518 cos(628t) +      5.1251 sin(628t)
```

7) Check your results in CircuitLab using a transient simulation for 50ms (time step = 50us).

The amplitude matches calculations

```
>> abs(V)
V0 10.0000
V1 8.6387
V2 7.0341
V3 5.3549
```

