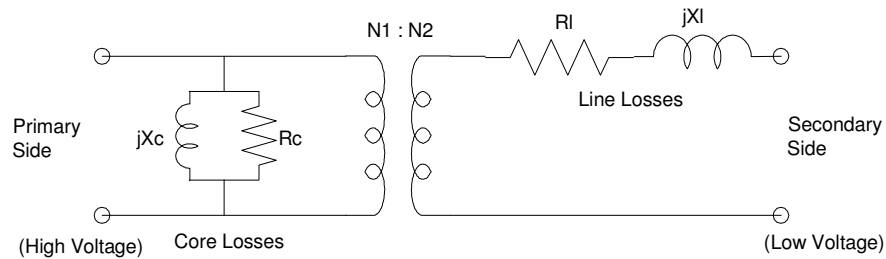


ECE 111: Homework 16

ECE 331 Energy Conversion
Due Monday, May 12th. Please submit via email or on BlackBoard

1) Determine the circuit model for a 13.2kV : 240V transformer is tested with the following test results:



Transformer Model

	V	Power	pf
Open-Circuit Test	$V_1 = 13.2\text{kV}$	20 W	0.01
Short-Circuit Test	$V_2 = 24\text{V}$	25 W	0.98

Core Model (open-circuit test)

```
>> V = 13.2e3;
>> P = 20;
>> pf = 0.01;
>> I = P / (V * pf)

I =    0.1515

>> Z = (V/I) * exp(j*acos(pf))

Z =  8.7120e+002 +8.7116e+004i
```

This is the series model. The parallel model comes from the inverse of Z

```
>> 1/Z

ans =  1.1478e-007 -1.1478e-005i

>> Rc = 1 / real(1/Z)

Rc =  8.7120e+006

>> Xc = -1 / imag(1/Z)

Xc =  8.7124e+004


>>
```

Line Model (short-circuit test)

```
>> V = 24;  
>> P = 25;  
>> pf = 0.98;  
>> I = P / (V * pf)  
  
I = 1.0629  
  
>> Z = (V/I) * exp(j*acos(pf))  
  
Z = 22.1276 + 4.4932i  
  
>> RL = real(Z)  
  
RL = 22.1276  
  
>> XL = imag(Z)  
  
XL = 4.4932
```

For the utility grid on the back of the page....

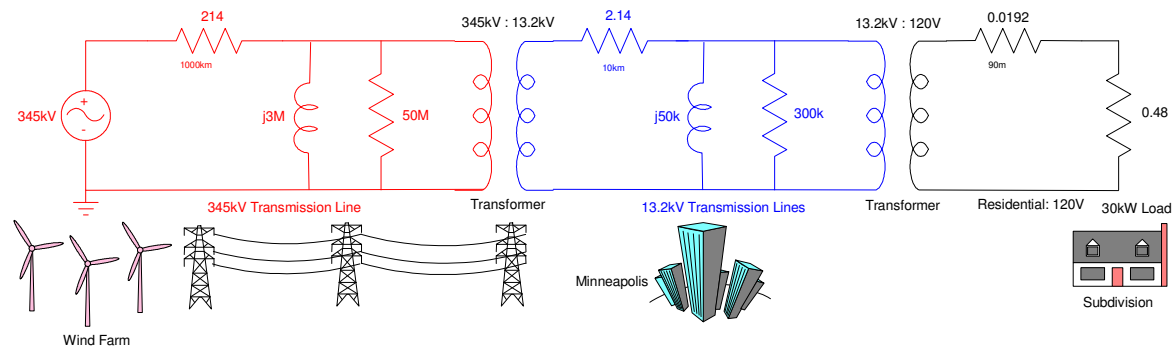
2) Convert the voltages and impedances to the 120V node (right side)



$$\begin{aligned}
 R01 &= 214 * (120/345e3)^2 \\
 X1 &= j*3e6 * (120/345e3)^2 \\
 R1 &= 50e6 * (120/345e3)^2 \\
 R12 &= 2.14 * (120/13.2e3)^2 \\
 R2 &= 300e3 * (120/13.2e3)^2 \\
 X2 &= j*50e3 * (120/13.2e3)^2 \\
 R23 &= 0.0192 \\
 R3 &= 0.48
 \end{aligned}$$

$$\begin{aligned}
 R01 &= 2.5890e-005 \\
 X1 &= 0 + 0.3629i \\
 R1 &= 6.0491 \\
 R12 &= 1.7686e-004 \\
 R2 &= 24.7934 \\
 X2 &= 0 + 4.1322i \\
 R23 &= 0.0192 \\
 R3 &= 0.4800
 \end{aligned}$$

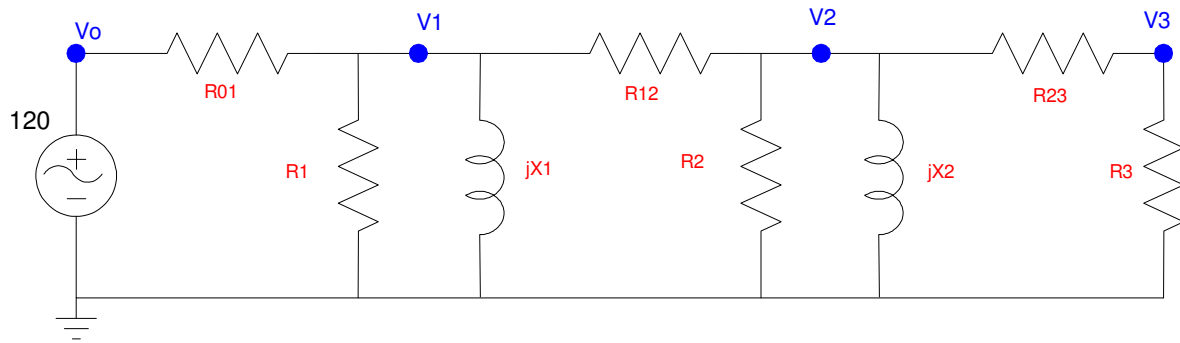3) Write the voltage node equations for this circuit (with transformers removed)



$$V_0 = 120$$

$$\left(\frac{V_1 - V_0}{R_{01}} \right) + \left(\frac{V_1}{R_1} \right) + \left(\frac{V_1}{jX_1} \right) + \left(\frac{V_1 - V_2}{R_{12}} \right) = 0$$

$$\left(\frac{V_2 - V_1}{R_{12}} \right) + \left(\frac{V_2}{R_2} \right) + \left(\frac{V_2}{jX_2} \right) + \left(\frac{V_2 - V_3}{R_{23}} \right) = 0$$

$$\left(\frac{V_3 - V_2}{R_{23}} \right) + \left(\frac{V_3}{R_3} \right) = 0$$

4) Determine the voltages at each node

Group terms

$$V_0 = 120$$

$$-\left(\frac{1}{R_{01}}\right)V_0 + \left(\frac{1}{R_{01}} + \frac{1}{R_1} + \frac{1}{jX_1} + \frac{1}{R_{12}}\right)V_1 - \left(\frac{1}{R_{12}}\right)V_2 = 0$$

$$-\left(\frac{1}{R_{12}}\right)V_1 + \left(\frac{1}{R_{12}} + \frac{1}{R_2} + \frac{1}{jX_2} + \frac{1}{R_{23}}\right)V_2 - \left(\frac{1}{R_{23}}\right)V_3 = 0$$

$$-\left(\frac{1}{R_{23}}\right)V_2 + \left(\frac{1}{R_{23}} + \frac{1}{R_3}\right)V_3 = 0$$

Place in matrix form

$$\begin{bmatrix} 1 & 0 & 0 & 0 \\ \left(\frac{-1}{R_{01}}\right) & \left(\frac{1}{R_{01}} + \frac{1}{R_1} + \frac{1}{jX_1} + \frac{1}{R_{12}}\right) & \left(\frac{-1}{R_{12}}\right) & 0 \\ 0 & \left(\frac{-1}{R_{12}}\right) & \left(\frac{1}{R_{12}} + \frac{1}{R_2} + \frac{1}{jX_2} + \frac{1}{R_{23}}\right) & \left(\frac{-1}{R_{23}}\right) \\ 0 & 0 & \left(\frac{-1}{R_{23}}\right) & \left(\frac{1}{R_{23}} + \frac{1}{R_3}\right) \end{bmatrix} \begin{bmatrix} V_0 \\ V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} 120 \\ 0 \\ 0 \\ 0 \end{bmatrix}$$

Solve in Matlab

```
R01 = 214 * (120/345e3)^2;
X1 = j*3e6 * (120/345e3)^2;
R1 = 50e6 * (120/345e3)^2;
R12 = 2.14 * (120/13.2e3)^2;
R2 = 300e3 * (120/13.2e3)^2;
X2 = j*50e3 * (120/13.2e3)^2;
R23 = 0.0192;
R3 = 0.48;

b1 = [1,0,0,0];
b2 = [-1/R01,1/R01+1/R1+1/X1+1/R12,-1/R12,0];
b3 = [0,-1/R12,1/R12+1/R2+1/X2+1/R23,-1/R23];
b4 = [0,0,-1/R23,1/R23+1/R3];
B = [b1;b2;b3;b4];
A = [120;0;0;0];
V = inv(B)*A

V0    120.00
V1    119.99 + 0.01i
V2    119.95 + 0.01i
V3    115.34 + 0.01i
```

The voltage at the customer has drooped down to 115.34 Volts

5) Determine the efficiency of this system

- Ignoring the core losses
 - Assumes a large number of customers share these losses
- Including the core losses

Assumes a single customer

```
V0 = V(1);
V1 = V(2);
V2 = V(3);
V3 = V(4);

P01 = abs(V0 - V1)^2 / R01
P1 = abs(V1)^2 / R1
P12 = abs(V1 - V2)^2 / R12
P2 = abs(V2)^2 / R2
P23 = abs(V2 - V3)^2 / R23
P3 = abs(V3)^2 / R3

eff = P3 / (P1 + P12 + P2 + P23 + P3)

eff = P3 / (P12 + P23 + P3)

P01 = 5.1660
P1 = 2380.2
P12 = 10.7756
P2 = 580.3140
P23 = 1108.5
P3 = 27713
```

The customer is using 27.7kW of power

The efficiency if you include everything is 87.17%

```
eff = P3 / (P1 + P12 + P2 + P23 + P3)
eff = 0.8717
```

The efficiency if you ignore the core losses (meaning their losses are distributed over a large number of customers) is 96.12%

```
eff = P3 / (P12 + P23 + P3)
eff = 0.9612
```

Transformers allow you to create a pretty efficient means of transporting electricity over large distances