

Homework #4: ECE 461 / 661

Code Composer Workbench, Mass Spring Systems, Rotational Systems

Code Composer Workbench / PLC Fiddle

note: For the PLC homework assignments, you can use either

- Allen Bradley's Code Composer Workbench along with a Micro810 PLC (lab kits available), or
- PLC Fiddle (plcfiddle.com)

It's kind of fun seeing and hearing the lights and relays opening and closing. PLC Fiddle is a lot more convenient, however, being an online site where there's nothing to download and install. Your pick.

1) Assume there are two 2-digit numbers, AB and CD, taking on the values of 0 to 3 (00 to 11).

Determine the logic for three outputs:


- X is true if $AB > CD$ *OUT-00 (red light) if using a Micro-810*
- Y is true if $AB == CD$ *OUT-01 (yellow light) if using a Micro-810*
- Z is true if $AB < CD$ *OUT-02 (green light) if using a Micro-810*

2) Implement these three outputs using ladder logic using Code Composer Workbench or PLC Fiddle

- It's kind of fun to see and hear the relays opening and closing with CCW and a Micro-810 PLC
- PLC Fiddle is a lot more convenient. You don't have to install anything.
- Your pick (you can use another program if you like)

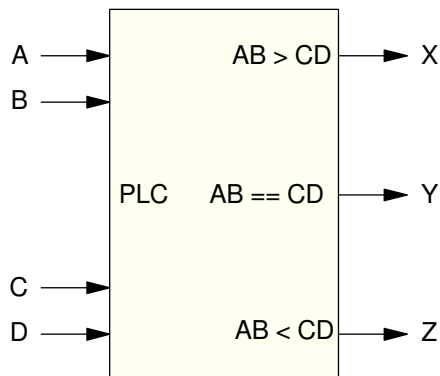
3) Demonstrate your working ladder logic program

- In-person, over zoom, attach a short video, take some screen shots



Mass-Spring Systems

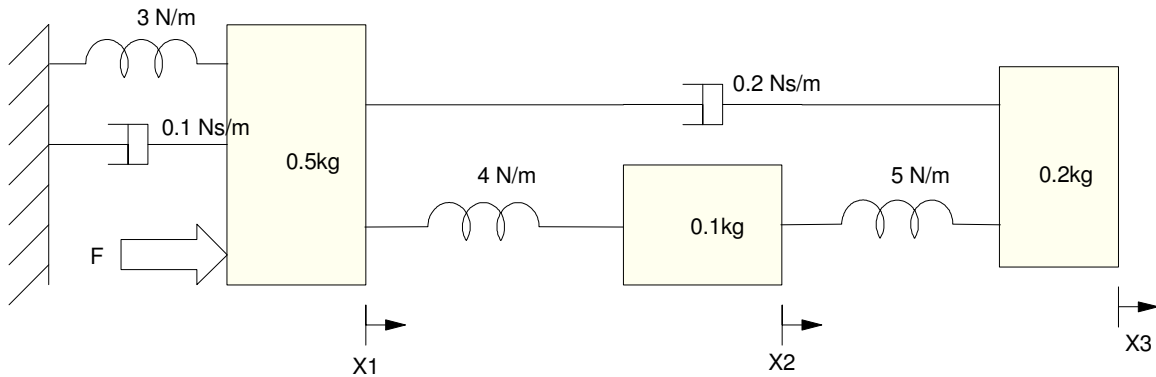Consider the following mass-spring system:




- 4) Draw the circuit equivalent for this system
- 5) Write the differential equations which describe this system
 - i.e. Write the voltage node equations.
- 6) Find the transfer function from F to x_3
- 7) Assume $F = 0$ and $x_3(0) = 1$ meter. What initial condition on x_1 and x_2 result in the energy in the system decaying
 - As fast as possible?
 - As slow as possible?

Rotational Systems

Assume for the following rotational system

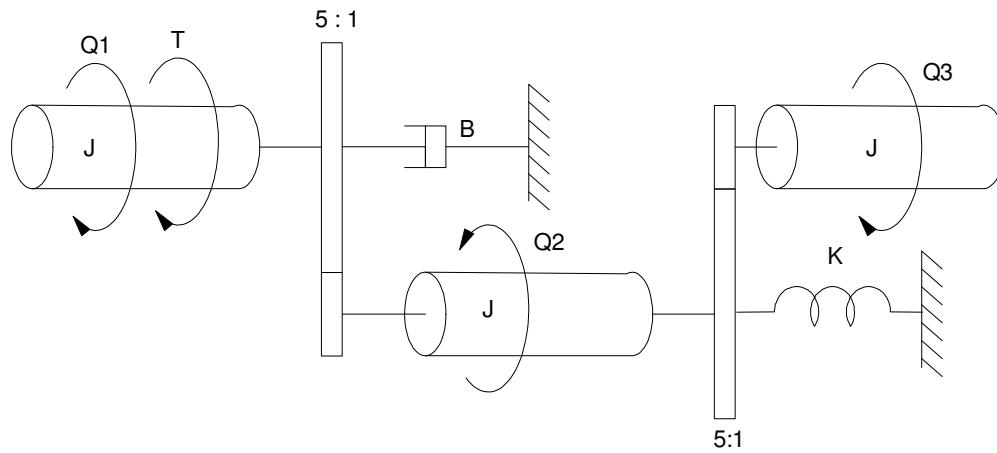- $J = 0.1 \text{ kg m}^2$
- $K = 2 \text{ Nm / radian}$
- $B = 0.1 \text{ Nms / radian}$



8) Draw the circuit equivalent for this system

9) Translate all of the impedances over to angle Q_1 and write the differential equations which describe this system.

10) Find the transfer function from T to Q_1