
Superposition

ECE 211 Circuits I

Lecture #12

Please visit [Bison Academy](#) for corresponding lecture notes, homework sets, and solutions

Superposition

- A circuit composed of resistors, inductors, capacitors, voltage sources, current sources, and dependent sources is a linear system.
- Linear systems have the property

$$f(a + b) = f(a) + f(b)$$

Meaning....

- If a circuit has two or more inputs,
- You treat this as two separate circuits, each with just one of the inputs.
- The net voltages (and currents) will be the sum of the separate problems

This is called *superposition*

Example 1:

$$V_0 = 10$$


$$\left(\frac{V_1 - V_0}{10}\right) + \left(\frac{V_1}{100}\right) + \left(\frac{V_1 - V_2}{20}\right) = 0$$

$$\left(\frac{V_2 - V_1}{20}\right) + \left(\frac{V_2}{200}\right) + \left(\frac{V_2 - V_3}{30}\right) = 0$$

$$\left(\frac{V_3 - V_2}{30}\right) + \left(\frac{V_3}{300}\right) + \left(\frac{V_3 - V_4}{40}\right) = 0$$

$$\left(\frac{V_4 - V_3}{40}\right) + \left(\frac{V_4}{400}\right) = 0$$

$$V_4 = 5$$

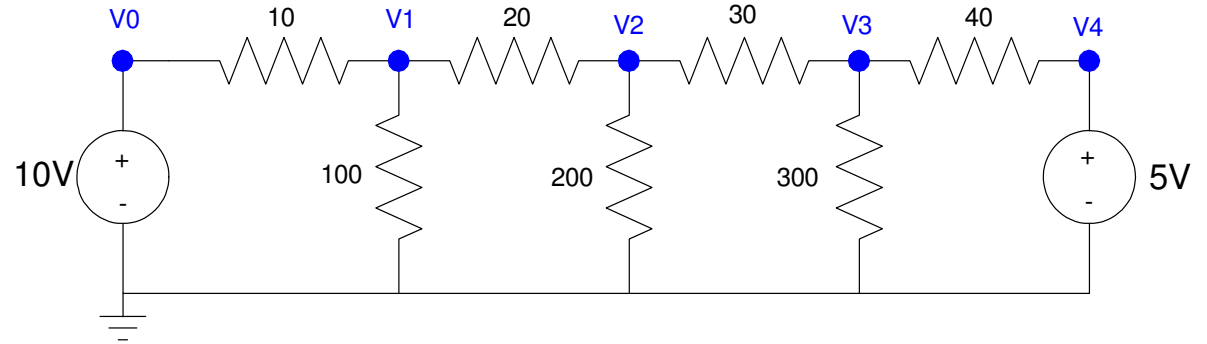


Result

	V0	V1	V2	V3	V4
V0 = 10V V4 = 5V	10.00 V	8.42 V	6.95 V	5.78 V	5.00 V

Superposition (take 1):

- $V_0 = \text{on}$
- $V_4 = \text{off}$


	V_0	V_1	V_2	V_3	V_4
$V_0 = 10\text{V}$ $V_4 = 0\text{V}$	10.00V	8.04 V	5.71 V	3.09 V	0.00 V

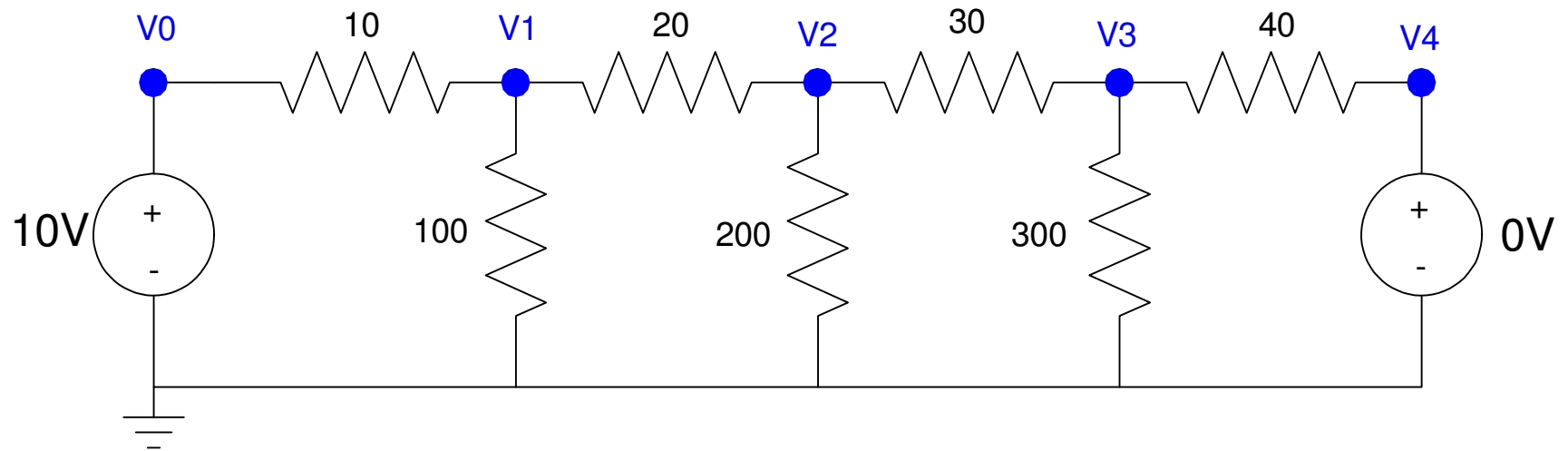

Superpositon (take 2)

- V0 = off
- V4 = on

	V0	V1	V2	V3	V4
V0 = 0V V4 = 5V	0.00 V	0.386 V	1.24 V	2.69 V	5.00 V

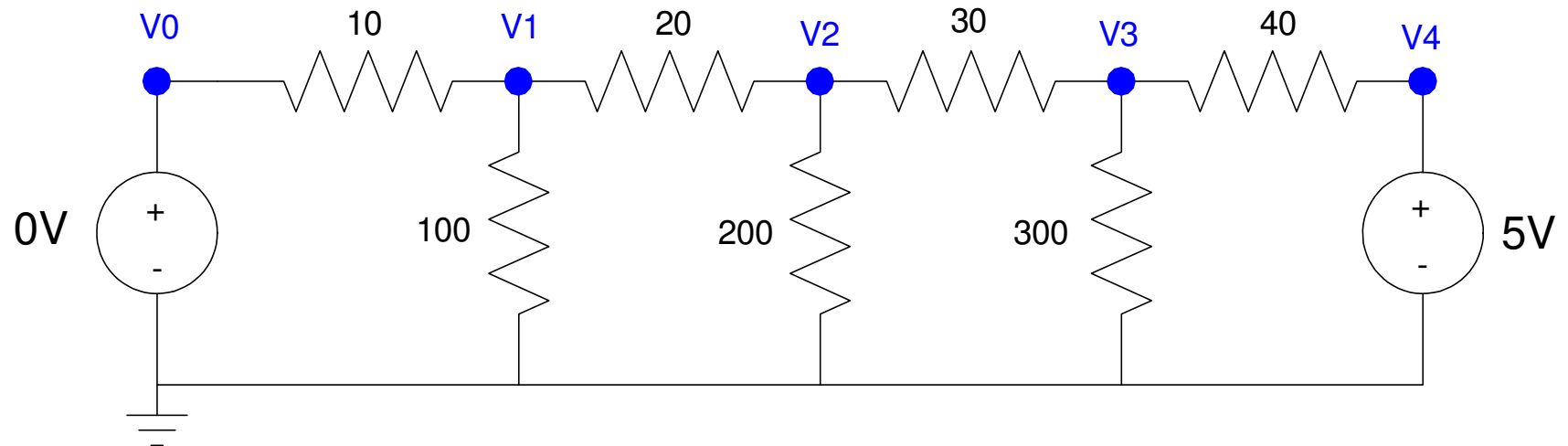

Superposition (take 3)

Note that the voltages add up


	V0	V1	V2	V3	V4
V0 = 10V, V4 = 0V	10.00V	8.04 V	5.71 V	3.09 V	0.00 V
V0 = 0V V4 = 5V	0.00 V	0.386 V	1.24 V	2.69 V	5.00 V
V0 = 10V V4 = 5V	10.00 V	8.42 V	6.95 V	5.78 V	5.00 V

Example 2: R-2R Ladder.

Determine Y as a function of A , B , C , and D

By superposition, we know that


$$Y = aA + bB + cC + dD$$

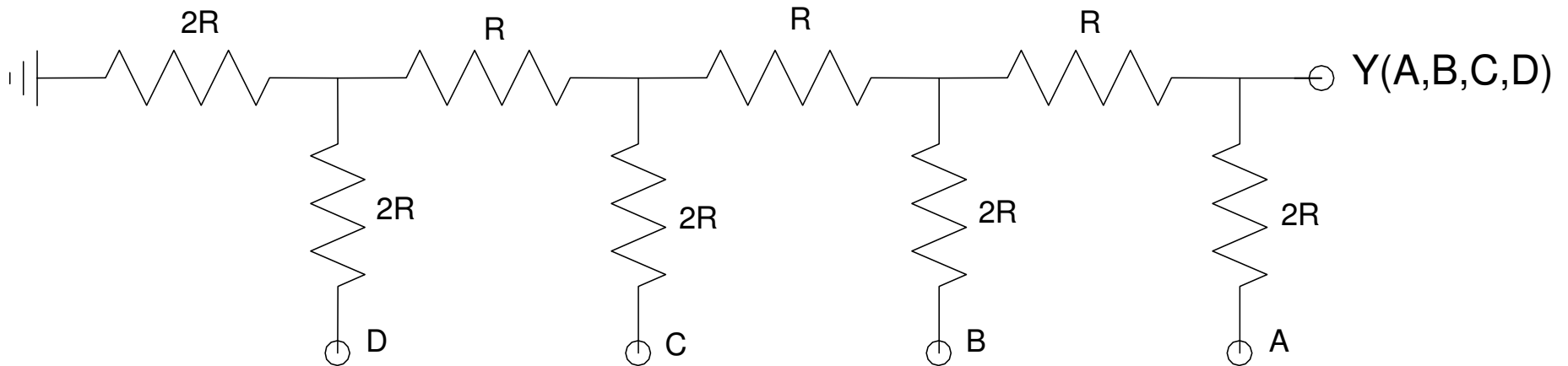

Case 1: $A = 1, B = C = D = 0.$

- Take the Thevenin equivalent of the circuit looking left at x. All you see is $2R \parallel 2R = R$ to ground.
- Repeat at y. All you see is $2R \parallel 2R = R$ to ground.
- Repeat at z. All you see is $2R \parallel 2R = R$ to ground.
- By voltage division, $Y = 1/2$ volt.


$$a = 1/2$$

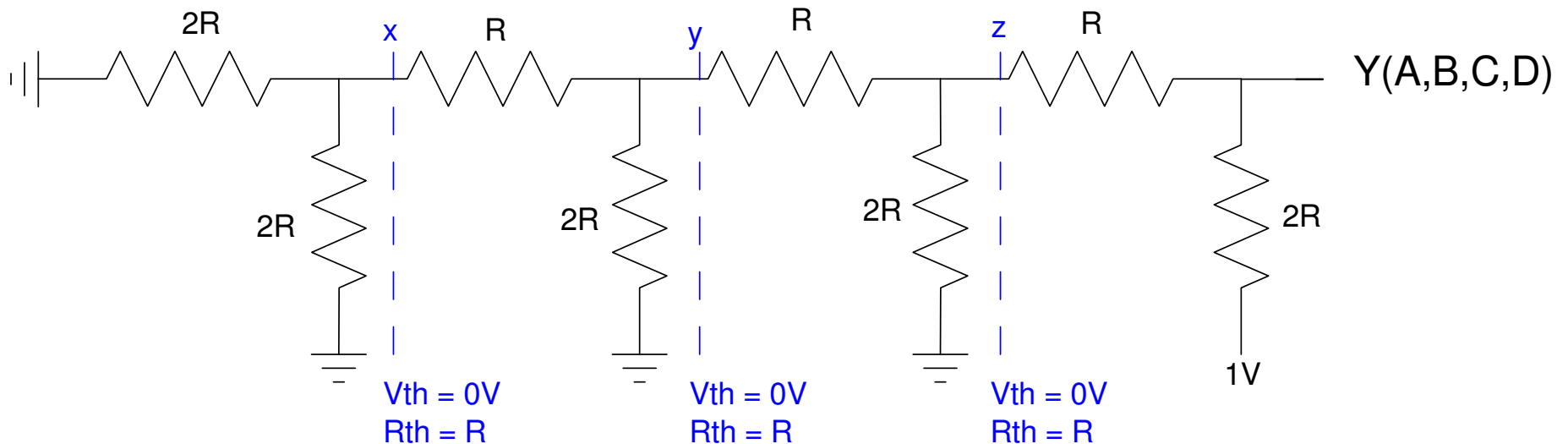

Case 2: $A = 0$, $B = 1$, $C = D = 0$.

- At w looking left, all you see is $2R \parallel 2R = R$
- At x looking left, all you see is $2R \parallel 2R = R$
- At y looking left, all you get
 - $R_{th} = 2R \parallel 2R = R$ $V_{th} = 1/2 V$
- At z looking left, you get
 - $R_{th} = 2R \parallel 2R = R$ $V_{th} = 1/2 * 1/2 = 1/4$

$$b = 1/4$$

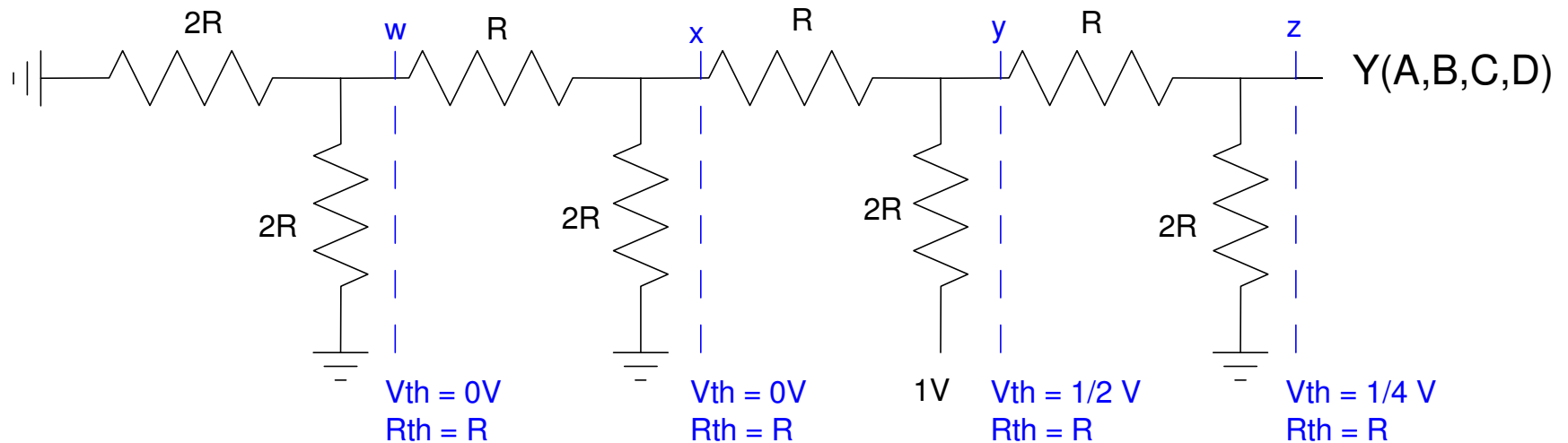


Case 3: $A = B = D = 0$. $C = 1$.

Taking the Thevenin equivalents looking left, you wind up with

- $Y = 1/8 \text{ V}$ ($c = 1/8$)

Similarly


- $d = 1/16$

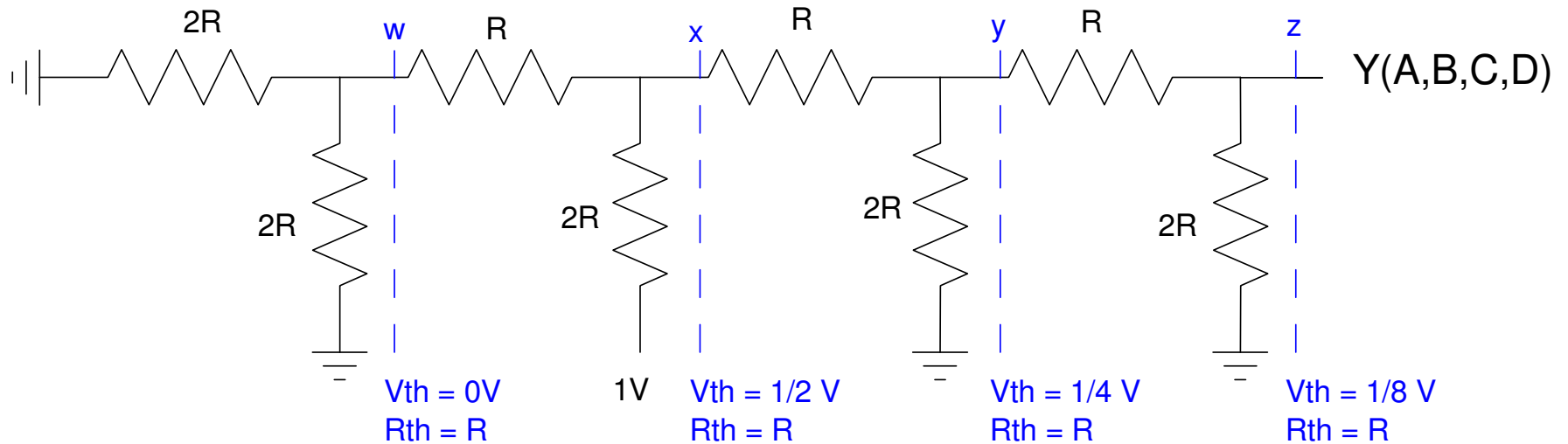

Net Result



$$Y = \left(\frac{1}{2}\right)A + \left(\frac{1}{4}\right)B + \left(\frac{1}{8}\right)C + \left(\frac{1}{16}\right)D$$

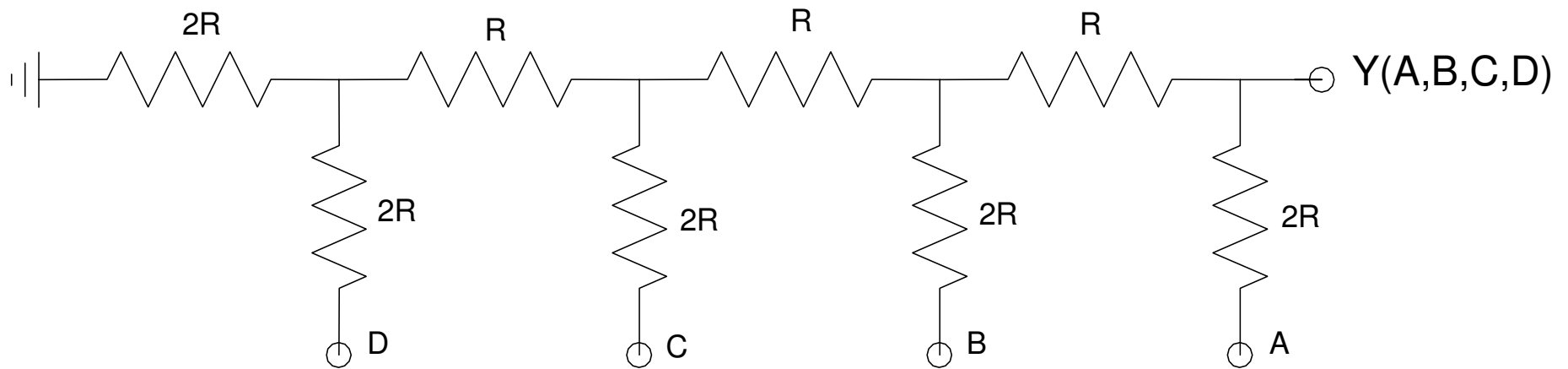- This circuit converts a binary number into an analog voltage





Checking in CircuitLab

- Gain from A is $1/2$

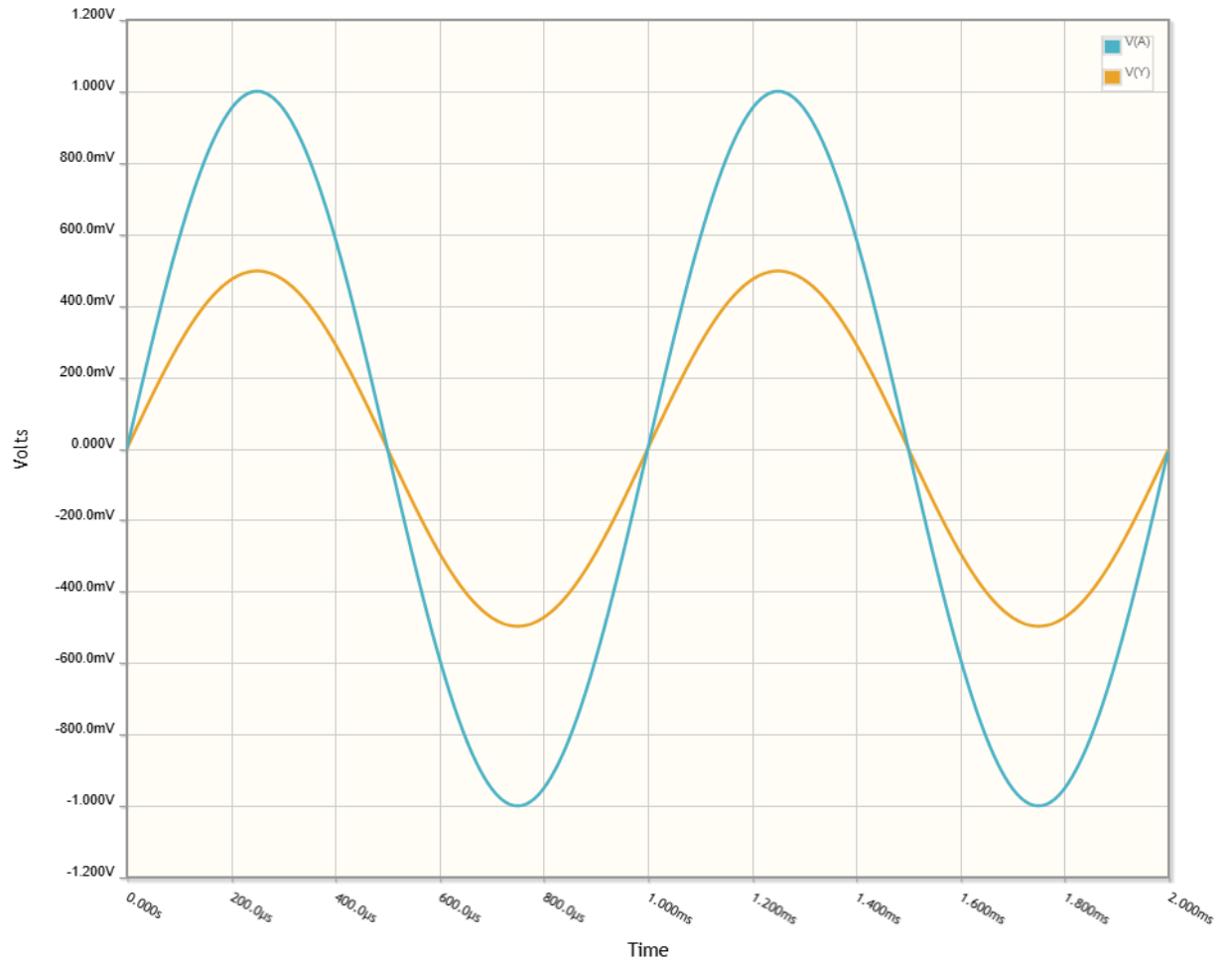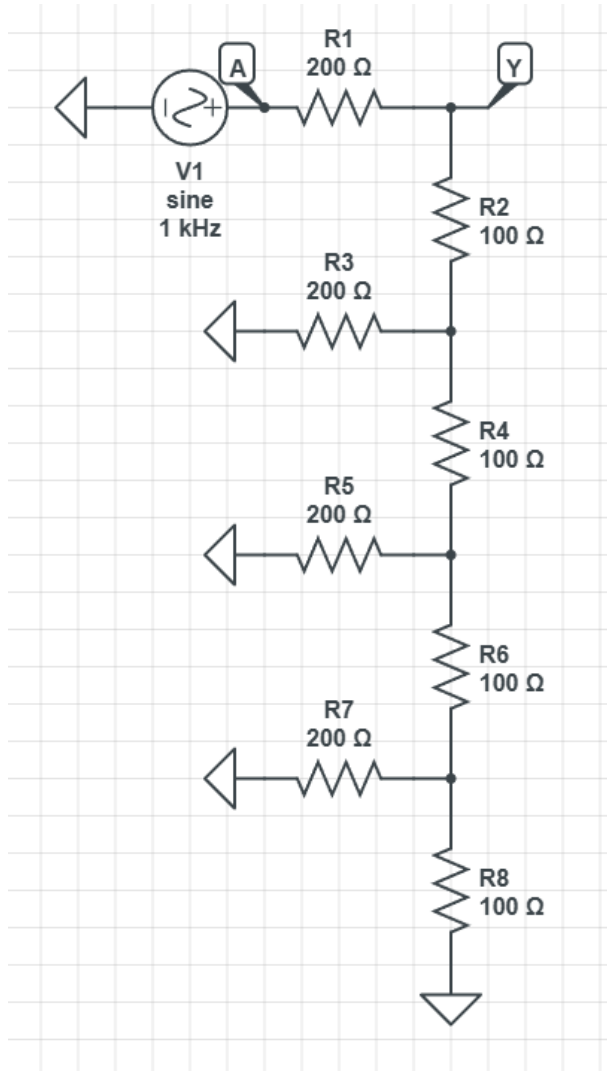



Checking in CircuitLab

Gain from B is 1/4

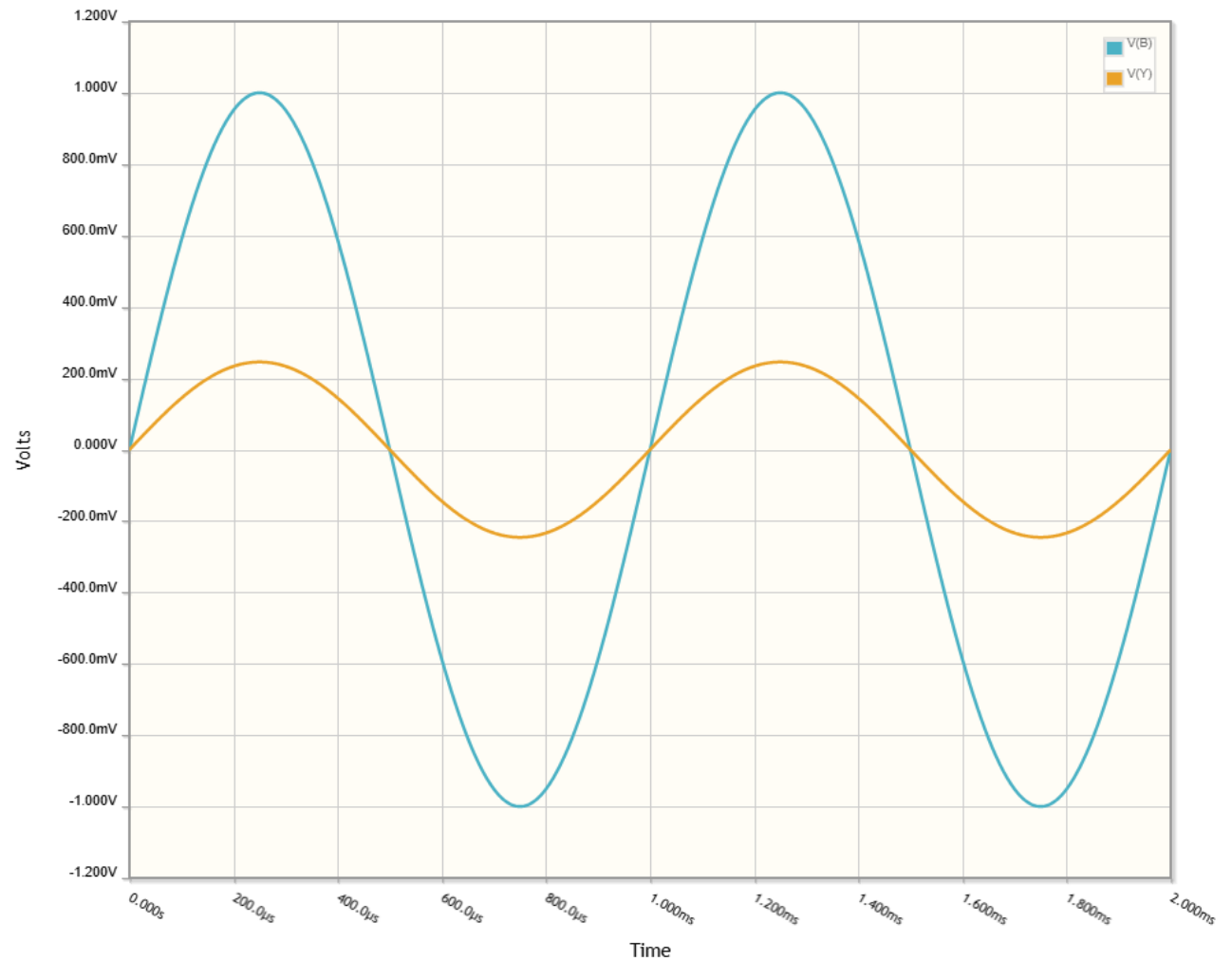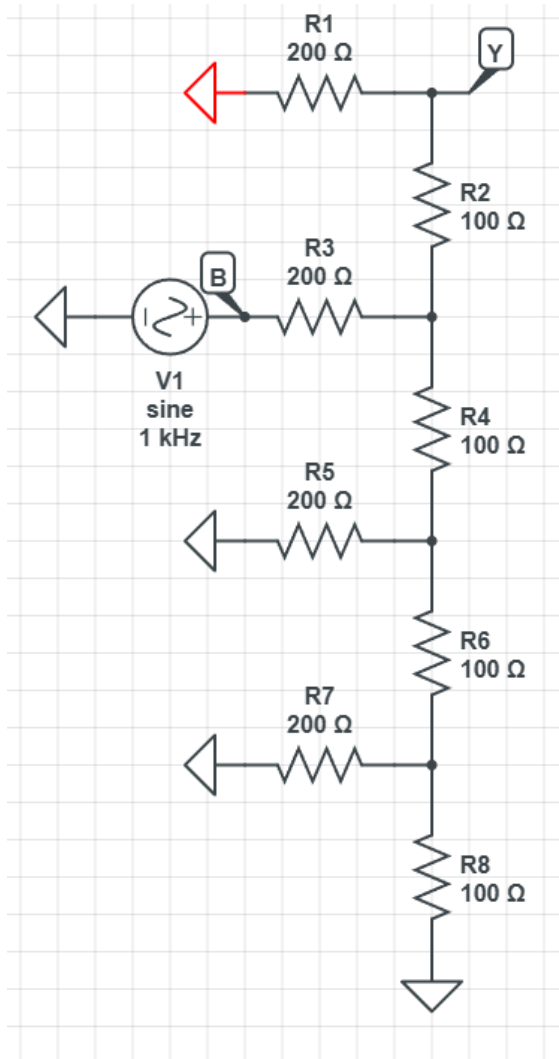



Checking in CircuitLab

- Gain from C is 1/8

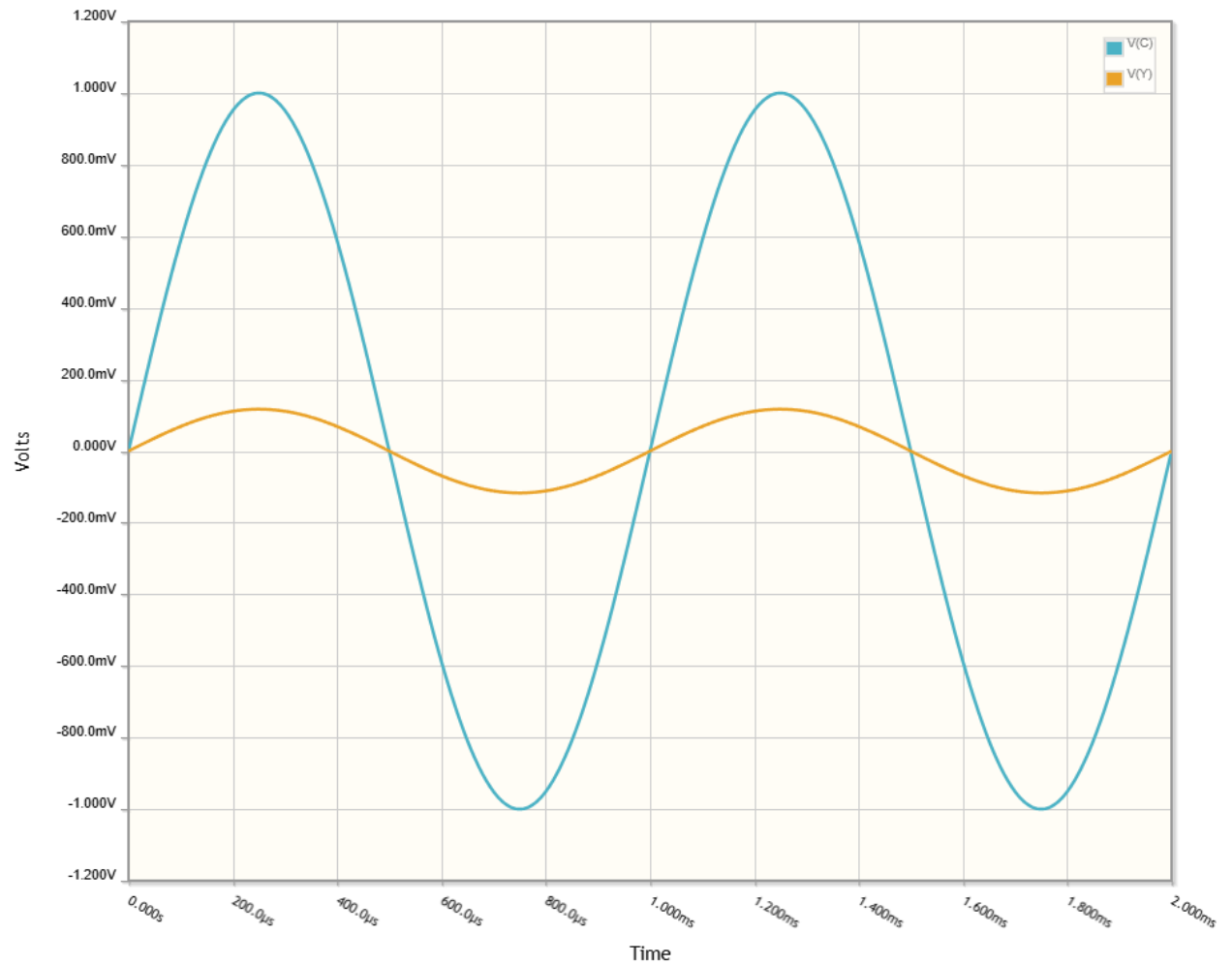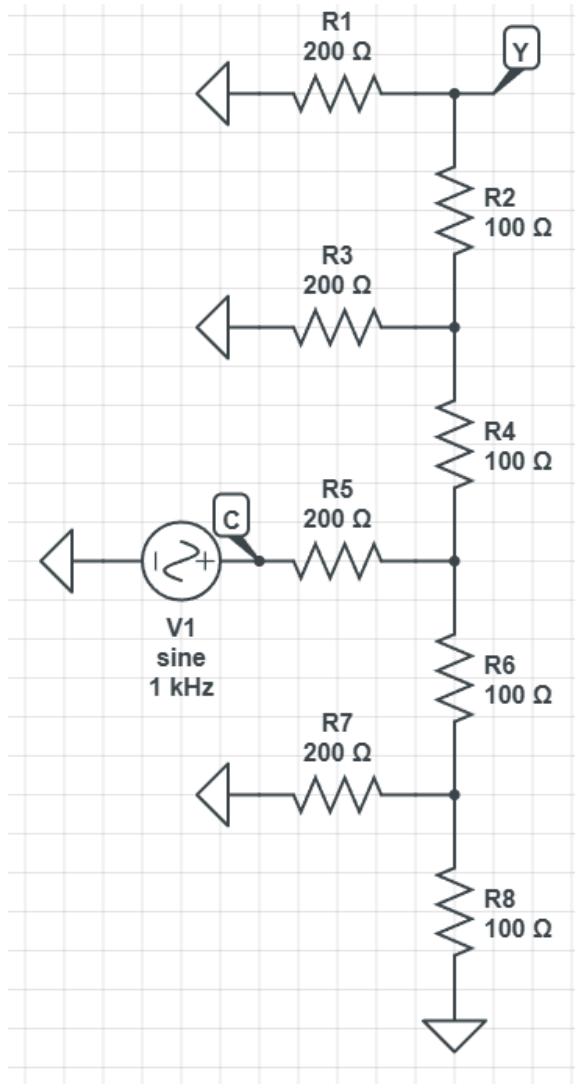

Checking in CircuiLab

- Gain from D is 1/16

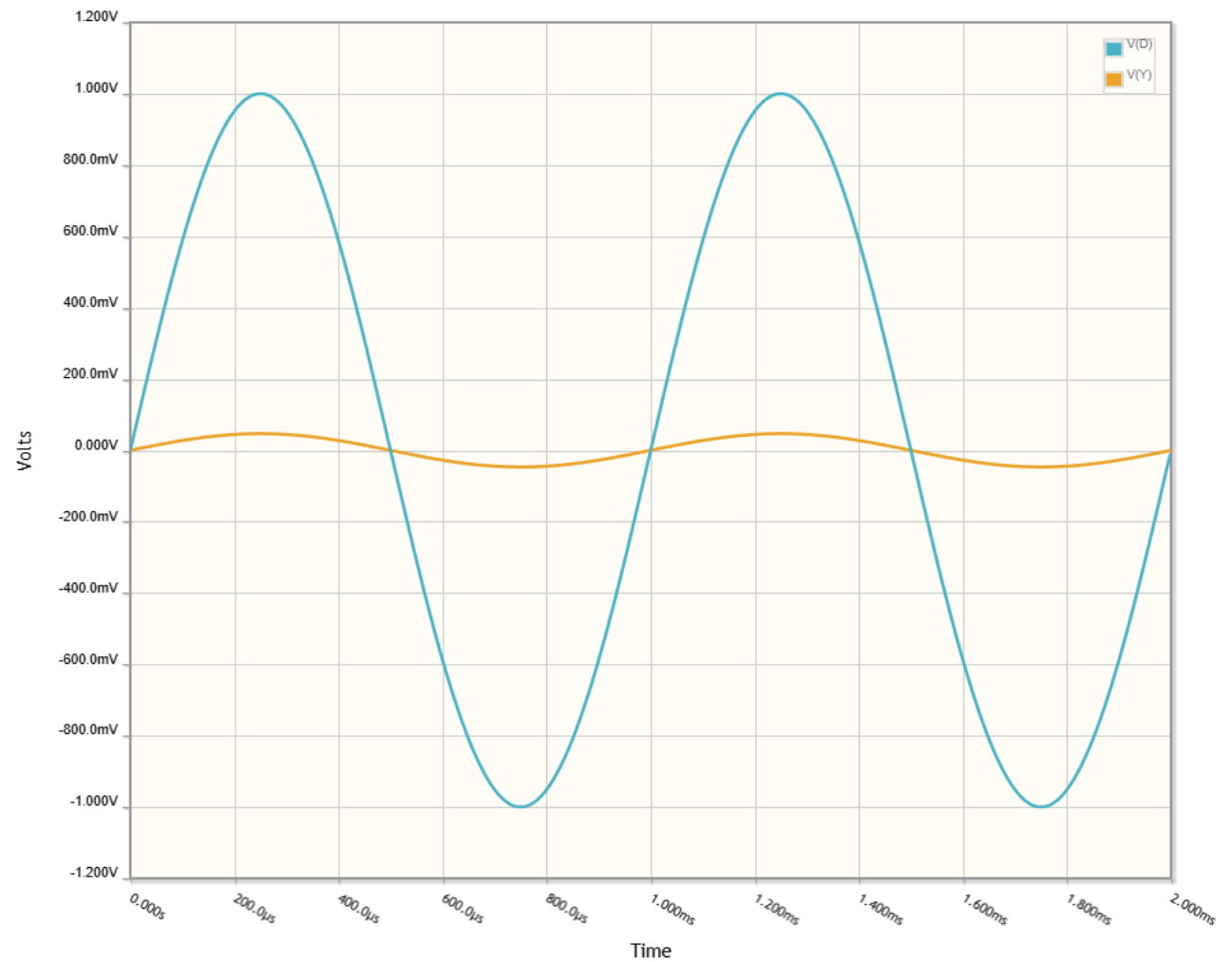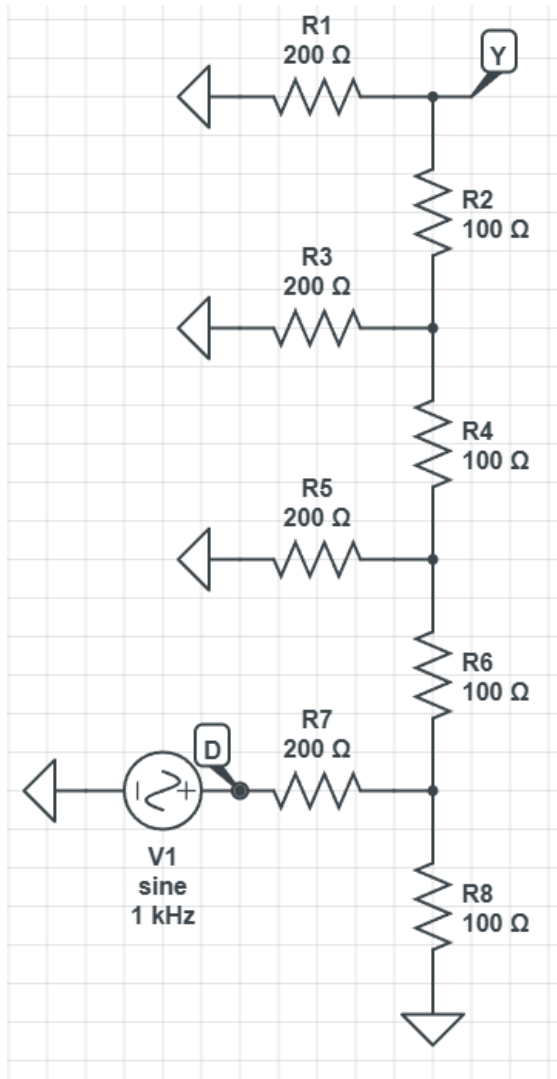

Example 3: Weighted Average

Case 1: Design a circuit so that Y is the average of $\{ A, B, C \}$


$$Y = \left(\frac{A+B+C}{3} \right)$$

By symmetry, use three resistors:

$$\left(\frac{Y-A}{R} \right) + \left(\frac{Y-B}{R} \right) + \left(\frac{Y-C}{R} \right) = 0$$

$$3Y = A + B + C$$


$$Y = \left(\frac{A+B+C}{3} \right)$$

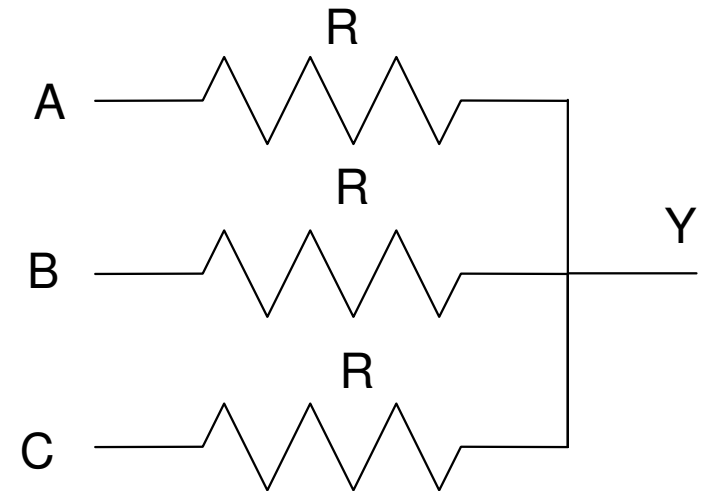

Case 2: Design a circuit so that Y is the weighted average:

$$Y = \left(\frac{2A+B+C}{4} \right)$$

Solution: Add A twice. This is equivalent to reducing R by 2:

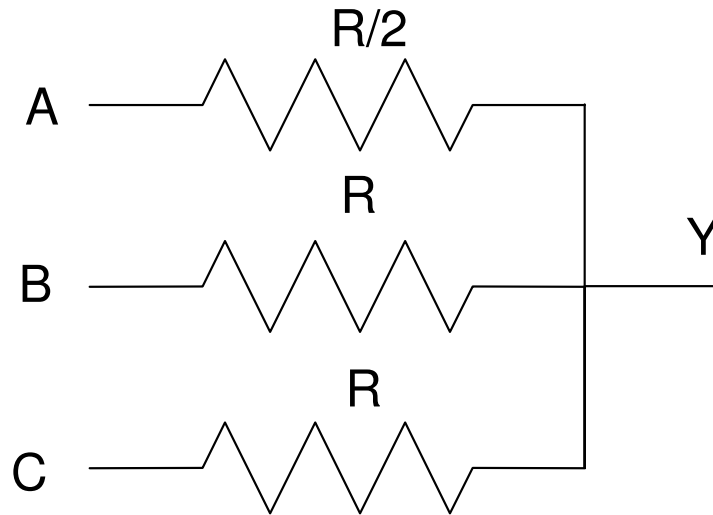


Case 3: Design a circuit to implement

$$Y = \left(\frac{aA + bB + cC}{a + b + c} \right)$$

Solution: Use a weighted average

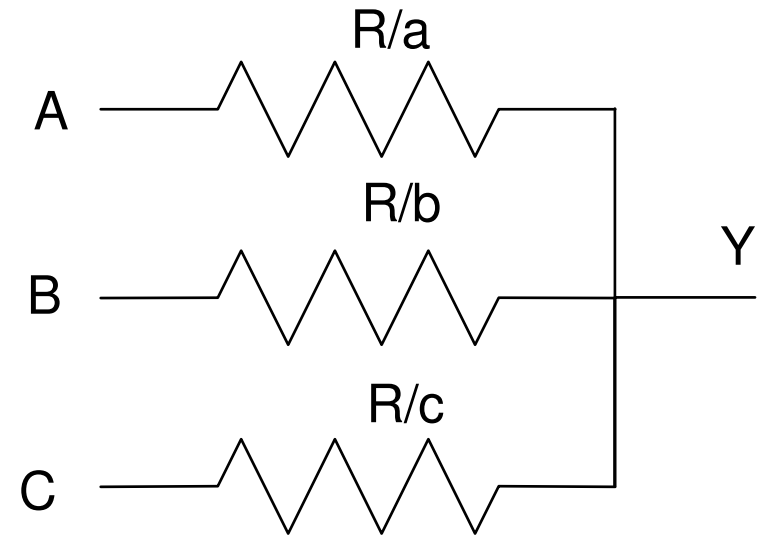
- Adjust the resistor by the weighting of A, B, and C



Sample Problem:

Find R's so that Y is the weighted average

$$Y = 0.2A + 0.65B + 0.1C + 0.05D$$

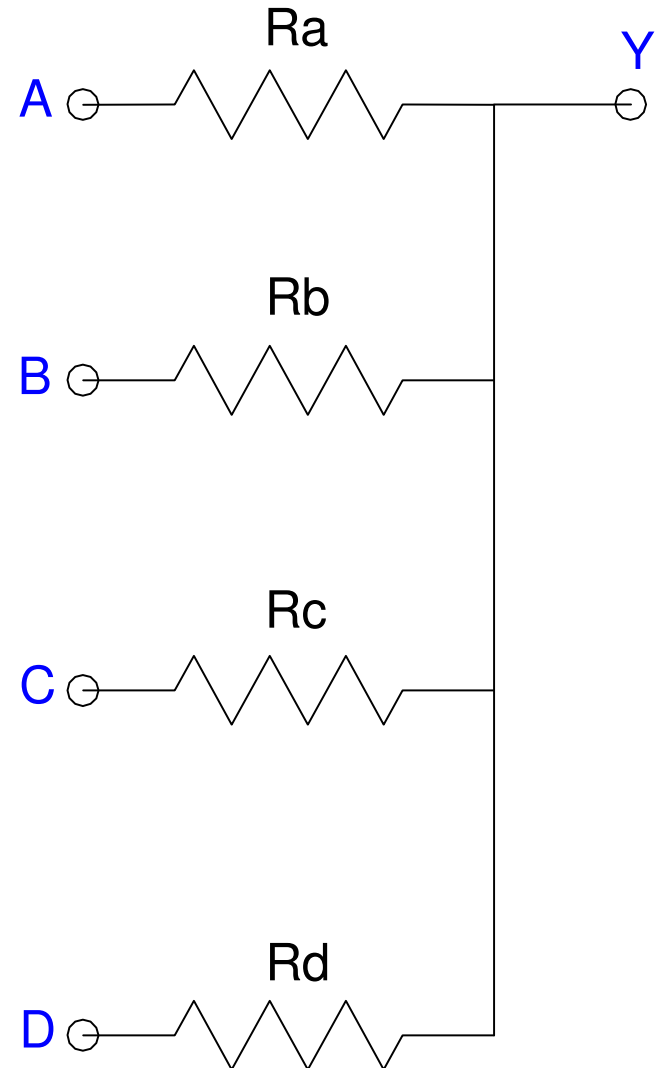

Example: Level Shifting

- Let A be an analog signal in the range of (-10V, +10V)

Design a circuit to shift this voltage to the range of 0..5V.


Solution: Y is related to A as

$$Y = \frac{1}{4}A + 2.5$$

Rewrite as



$$Y = \frac{1}{4}A + \frac{1}{2}(5V) + \frac{1}{4}(0V)$$
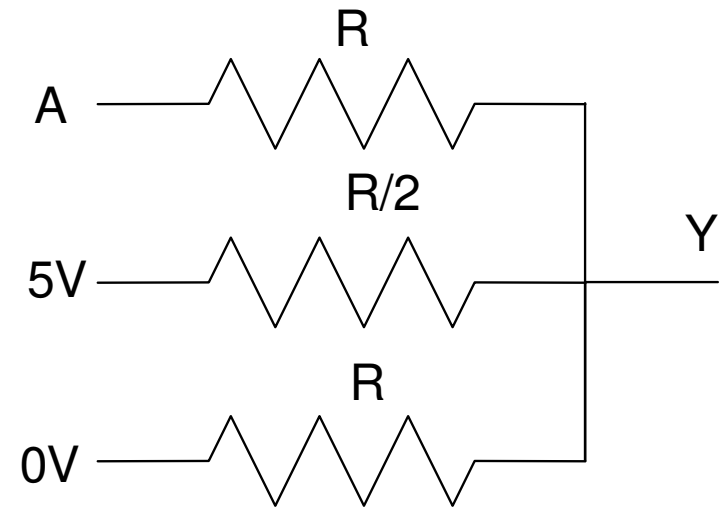
$$Y = \left(\frac{1 \cdot (A) + 2 \cdot (5V) + 1 \cdot (0V)}{4} \right)$$



Checking in CircuitLab

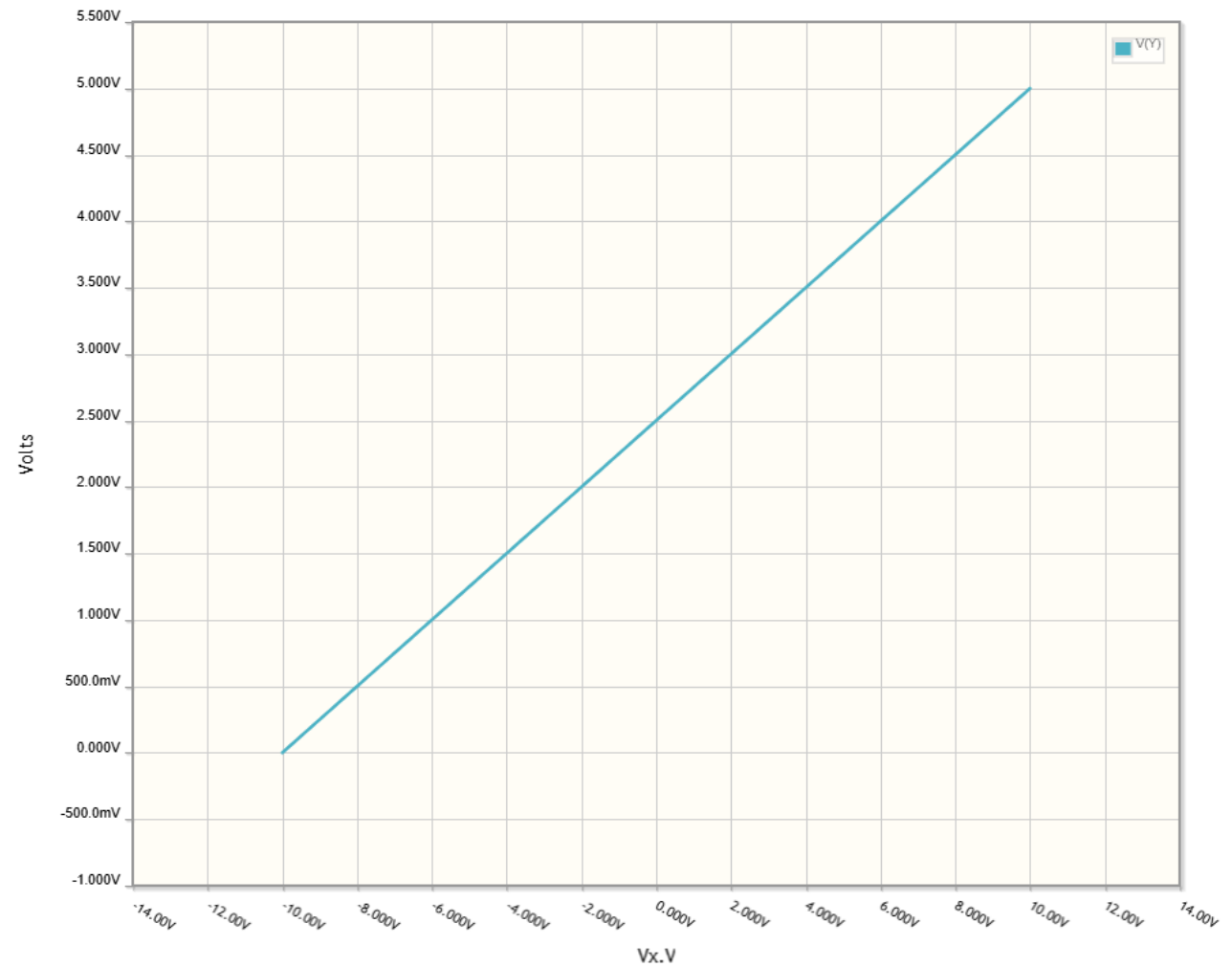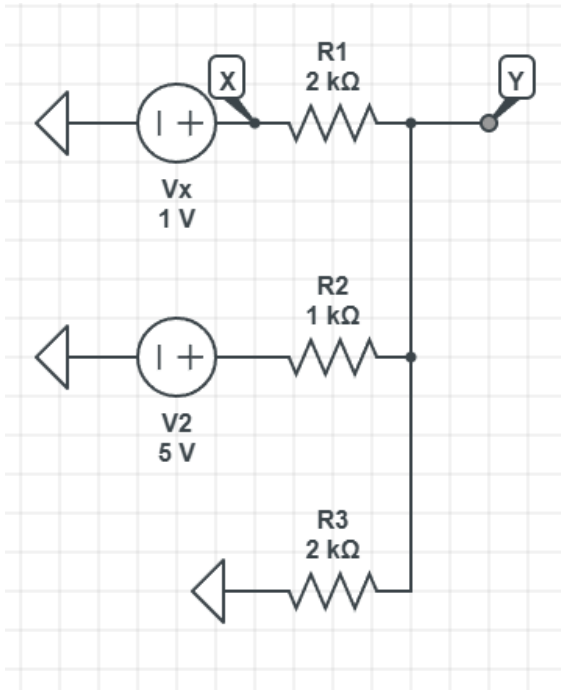- DC Sweep V_x from -10V to +10V
- V_y goes 0V to 5V



Practice Problem

Find R's so that this circuit converts


- -5V to +5V (X)

to

- 0V to +3.3V

$$Y = \left(\frac{3.3}{10}\right)X + 1.65$$

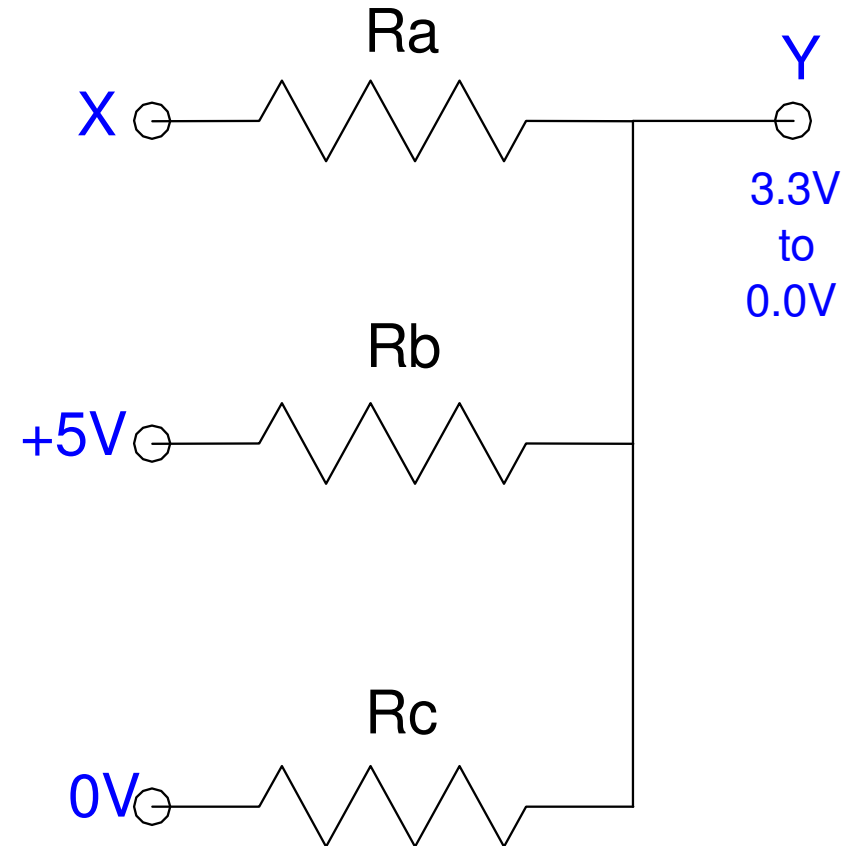Assume you have signals {X, +5V, 0V} to work with



Summary

Resistor circuits are linear

$$f(a + b + c) = f(a) + f(b) + f(c)$$

This means that, if you have several inputs

- You can turn on the inputs one at a time
- Find the output for that input
- Then sum the results to get the output for all inputs turned on.

This is called *superposition*
